

# EE3235 Analog Integrated Circuit Analysis and design I

## Homework 4


### Ideal OP circuit

110061217 王彦智

PART1 : Design the amplifier in Fig. 2

#### 1. Ideal operational amplifier simulation
 
##### 1. Calculation of ideal opamp simulation



$$\begin{aligned} V_{out} &= -A_o V_x \rightarrow V_x = \frac{-1}{A_o} V_{out} \\ \frac{V_x - V_{in}}{R_1} &= \frac{V_{out} - V_x}{R_2} \quad \dots (2) \\ \therefore \frac{-\frac{1}{A_o} V_{out} - V_{in}}{R_1} &= \frac{V_{out} - \frac{-1}{A_o} V_{out}}{R_2} \end{aligned}$$

$$\rightarrow g_{am} = \frac{V_{out}}{V_{in}} = \frac{-1}{\frac{R_1}{R_2} + \frac{1}{A_o} (1 + \frac{R_1}{R_2})} \quad \therefore 9.8 \leq \frac{1}{\frac{R_1}{R_2} + \frac{1}{A_o} (1 + \frac{R_1}{R_2})} \leq 10.2$$


$$\therefore \frac{R_2}{R_1} = 19 \rightarrow \frac{R_1}{R_2} = 0.1$$

$$\therefore 9.8 \leq \frac{1}{0.1 + 1.1(\frac{1}{A_o})} \leq 10.2 \rightarrow A_o \geq 539 \text{ or } A_o \leq -561 (x)$$

$\therefore$  do hspice simulation to check if  $A_o = 539$  achieve the SPEC


Hand calculation.

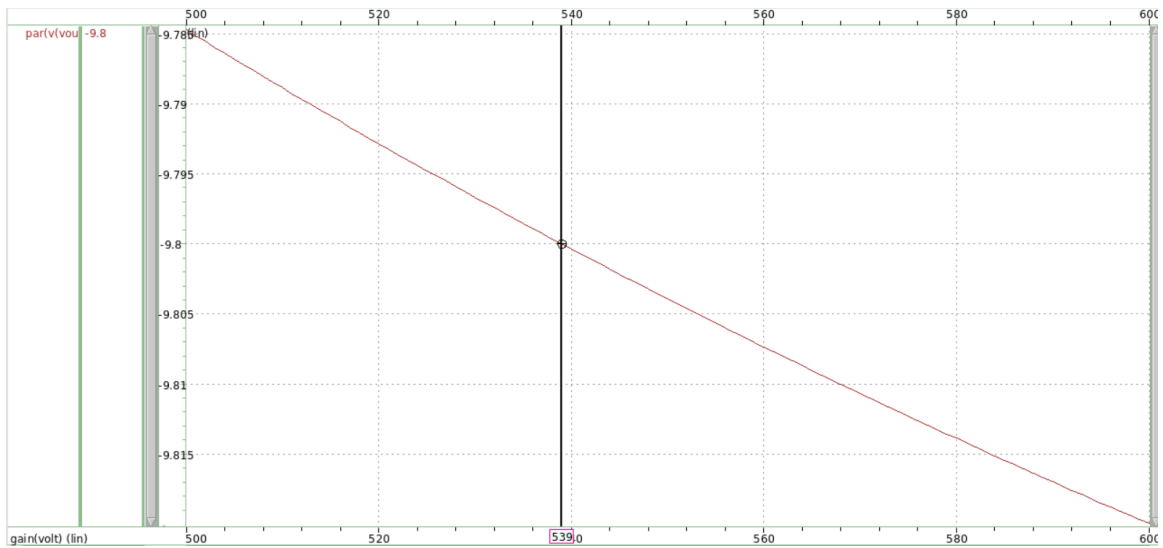To verify the results, I run Hspice with an ideal amplifier(E) and two resistor ( $R_1=1k\Omega$ ,  $R_2=10k\Omega$ ) and sweep the gain of ideal amplifier from 500 to 600 to see when close loop gain equals 9.8(v/v).



X axis: open loop gain(V/V)-Y axis: closed loop gain(V/V)

## 2. Circuit Design

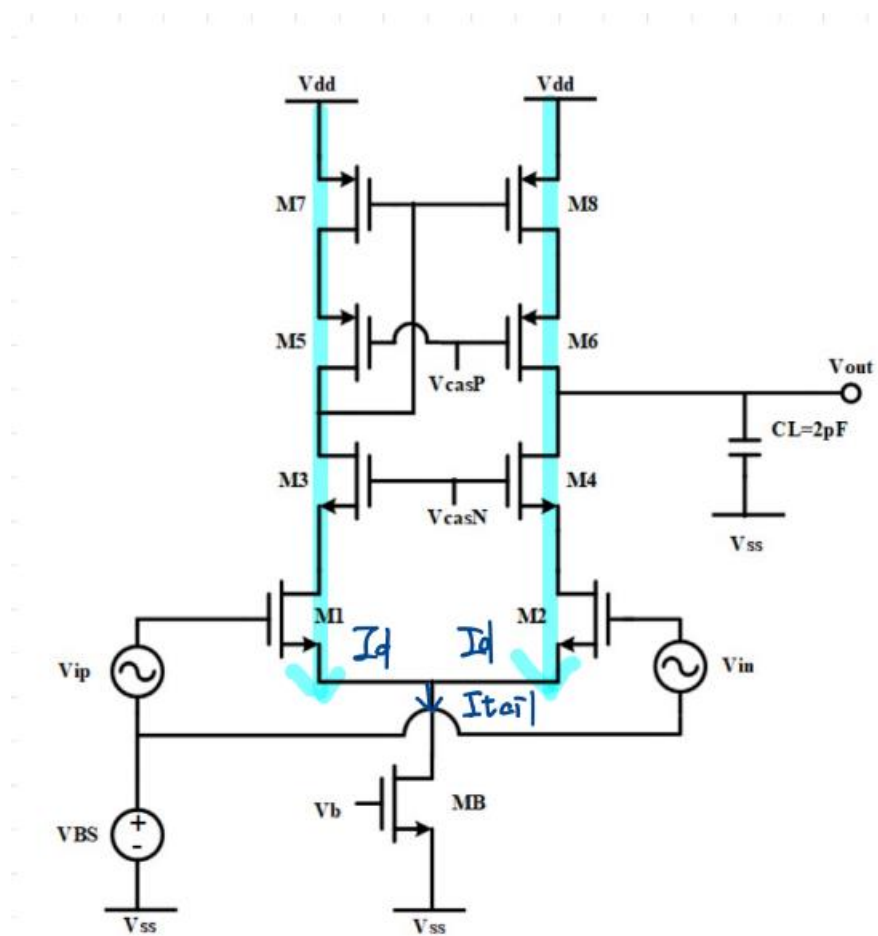

Step1. Check out the speculation and circuit architecture.

- All NMOS and PMOS should be in saturation region.

- Gain should be larger than 539(V/V)
- -3dB bandwidth should be larger than 7kHz
- Symmetric circuit: minimize common mode noise.
- Cascade: increase output gain

Step 2. Simplify estimation and calculation

- Make length and width of M1 to M8 same, so W/L of all transistor are same, all NMOS parameters (e.g. beta value) are same, and also all PMOS parameters are same
- Tail current is decided by MB and Vb, so I replaced it by an ideal current source (after determine current value, I will change it back). And so:

Step 3. Gain bandwidth and power calculations.

### 3. Gain, Bandwidth and Power calculation

$$A_{\text{gain}} = g_{m2} R_{\text{out}}$$

$$= \frac{2 I_d}{V_{B3} - V_X - V_{th}} \left( \frac{2 I_d}{V_{asN} - V_6 - V_{th}} \cdot \frac{1}{I_d \lambda_4} \cdot \frac{1}{I_d \lambda_2} \parallel \frac{2 I_d}{V_{asp} - V_2 - V_{th}} \cdot \frac{1}{I_d \lambda_6} \cdot \frac{1}{I_d \lambda_8} \right)$$

$$= \frac{2 I_d}{V_{B3} - V_X - V_{th}} \left( \frac{2}{(V_{asN} - V_6 - V_{th}) I_d \lambda_4 \lambda_2} \parallel \frac{2}{(V_{asp} - V_2 - V_{th}) I_d \lambda_6 \lambda_8} \right)$$

$$= \frac{2 I_d}{V_{B3} - V_X - V_{th}} \cdot \frac{2}{I_d} \left( \frac{1}{(V_{asN} - V_6 - V_{th}) \lambda_4 \lambda_2} \parallel \frac{1}{(V_{asp} - V_2 - V_{th}) \lambda_6 \lambda_8} \right),$$

And:

$$V_{asN} - V_6 - V_{th} = \sqrt{\frac{2 I_d}{\mu_n C_{ox} \frac{W}{L}}}$$

$$V_{B3} - V_X - V_{th} = \sqrt{\frac{2 I_d}{\mu_n C_{ox} \frac{W}{L}}}$$

$$V_{asp} - V_2 - V_{th} = \sqrt{\frac{2 I_d}{\mu_p C_{ox} \frac{W}{L}}}$$

$$\textcircled{2} \text{ Bandwidth} \approx \text{dominant pole} = \frac{1}{R_{\text{out}} \cdot C_L}$$

$$= \frac{1}{\left( \frac{2 I_d}{V_{asN} - V_6 - V_{th}} \cdot \frac{1}{I_d \lambda_4} \cdot \frac{1}{I_d \lambda_2} \parallel \frac{2 I_d}{V_{asp} - V_2 - V_{th}} \cdot \frac{1}{I_d \lambda_6} \cdot \frac{1}{I_d \lambda_8} \right) \cdot C_L}$$

$$\textcircled{3} \text{ Power} : I_{D \text{ total}} \times V_{DD} = I_{D \text{ tail}} \times V_{DD}$$

Step 4. Choose the ideal current value (if I can't adjust a proper parameter to achieve the speculation in the following steps, I will go back to this step to increase the current a little bit):

choose an ideal current value  
by step3 the power =  $I_{dter1} \times V_{dd}$ , and I hope my  
power dissipation is about  $10\mu W$   
 $\therefore I_{dter1} = \frac{10\mu}{1.8} \approx 5.5 \rightarrow$  we  $I_{dter1} = 6\mu$ ,  $I_d = 3\mu$

Step 5. Choose size of NMOS and PMOS:


- L should not be too small, or the threshold voltage will be too large, and it will be more difficult to keep all transistors in saturation region
- I use the following test to check out the relationship between  $r_o$  ( $1/g_{ds}$ ) and W/L, we can see  $r_o$  is approximately proportional to W/L and from the gain and bandwidth equation in step3., if  $r_o$  increases(W/L increases), gain increases and bandwidth decreases, so we should let W/L a proper value so that gain will not be too small, and bandwidth will not be too small.
- I use the following test to check out the relationship between beta and W/L, we can see beta is approximately proportional to W/L and from the gain and bandwidth equation in step3., if beta increases(W/L increases), gain decrease and bandwidth increases, so we should let W/L a proper value so that gain will not be too small, and bandwidth will not be too small.
- Finally, I choose  $L=0.5\mu m$ ,  $W=2\mu m$

```
m1 vdd vb gnd gnd n_18 l=.5u w=2u  
m2 vdd vb gnd gnd n_18 l=.5u w=4u  
m3 vdd vb gnd gnd n_18 l=1u w=2u  
m4 vdd vb gnd gnd n_18 l=1u w=4u
```

subckt				
element	0:m1	0:m2	0:m3	0:m4
model	0:n_18.1	0:n_18.1	0:n_18.1	0:n_18.1
region	Saturation	Saturation	Saturation	Saturation
id	20.2036u	42.2446u	14.3959u	29.9079u
ibs	-4.493e-21	-7.796e-21	-3.202e-21	-5.519e-21
ibd	-384.9075a	-638.7762a	-384.9088a	-638.7785a
vgs	600.0000m	600.0000m	600.0000m	600.0000m
vds	1.8000	1.8000	1.8000	1.8000
vbs	0.	0.	0.	0.
vth	433.7470m	429.1863m	383.5547m	379.1470m
vdsat	170.9181m	173.8957m	198.5977m	201.8223m
vod	166.2530m	170.8137m	216.4453m	220.8530m
beta	1.2934m	2.5909m	621.5332u	1.2461m
gam_eff	507.4465m	507.4465m	507.4463m	507.4464m
gm	198.0789u	405.5012u	116.2023u	237.2249u
gds	2.7004u	5.5150u	1.2484u	2.5516u
gmb	36.4279u	74.5801u	22.1406u	45.1905u
cdtot	2.3923f	4.6882f	2.3927f	4.6889f
cgtot	7.3336f	14.6710f	13.7824f	27.5612f
cstot	9.0229f	17.9135f	15.5462f	30.9591f
cbtot	5.6081f	10.9787f	7.2572f	14.2758f
cgs	6.0299f	12.0690f	12.0137f	24.0318f
cgd	720.4754a	1.4412f	707.3906a	1.4150f

Step 6. Adjust bias voltage:  $V_{casn}$ ,  $V_{casp}$

 adjust bias  $V_b$   
 ideal case: if  $V_{th} \approx 0.45V$



so that all of transistor's  $V_{GS} - V_{th} = 0.6V$   
 but finally I found  $V_{casN}$  too large to  
 achieve the SPEC. so I decrease  $V_{casN}$   
 to 1 and finetune  $V_{casP}$   
 $\Rightarrow V_{casN} = 1V, V_{casP} = 0.85V$

Step 7. I found that adjust bias voltage will affect gain and bandwidth a lot, so if the gain or bandwidth is really closed to speculation, I will fin tune the size of M3 and M4.

7. why choose M3, M4 for tune?

1. can also adjust  $V_{casN}$ , since  $V_{casN}$  is connected to the gate of M3 and M4
  2.  $R_{out} = (R_{on} \parallel R_{op}) = (g_{m3}r_{o3}r_{o2}) \parallel (g_{m4}r_{o4}r_{o8})$   
so adjust M4 (or M3) and adjust two parameters at the same time ( $g_{m4}$  and  $r_{o4}$ )
  3. and since  $\mu_n > \mu_p$ ,  $g_{m3}r_{o3}r_{o2}$  is the main factor of  $(g_{m3}r_{o3}r_{o2}) \parallel (g_{m4}r_{o4}r_{o8})$  so I did choose M3, M4 to adjust
- W of M3 M4 become 0.45  
and  $V_{casN}$  become 1V finally

Step 8. Change the ideal current source back to a NMOS.

finally I achieved the SPEC, which current = 3uA is reasonable, so I change it back to an NMOS and fix the  $V_b$  and W of M<sub>b</sub> (L fixed to 0.5um) so that saturation current of M<sub>b</sub> is about 6uA  
→  $V_b = 0.45$  W = 6.8um  $I_{dsat} = 5.9680 \mu A$  (V)



```

vdd vdd 0 1.8
vss vss 0 0
vb vb 0 0.45
vn vcasn 0 1
vp vcasp 0 0.85

vcm vcm vss dc=0.9
vdiff vdiff vss dc=0 ac=1
Ep vip vcm vdiff vss 0.5
En vin vcm vdiff vss -0.5

mb vmb vb vss vss n_18 l=.5u w=6.8u
m1 vm1 vip vmb vss n_18 l=.5u w=2u
m2 vm2 vin vmb vss n_18 l=.5u w=2u
m3 vm3 vcasn vm1 vss n_18 l=.5u w=2.2u
m4 vout vcasn vm2 vss n_18 l=.5u w=2.2u
m5 vm3 vcasp vm7 vdd p_18 l=.5u w=2u
m6 vout vcasp vm8 vdd p_18 l=.5u w=2u
m7 vm7 vm3 vdd vdd p_18 l=.5u w=2u
m8 vm8 vm3 vdd vdd p_18 l=.5u w=2u

cl vss vout 2p

```

### Circuit design

subckt	0:m6	0:m7	0:m8
element	0:p_18.1	0:p_18.1	0:p_18.1
model	Saturation	Saturation	Saturation
region	id	id	id
id	-2.9840u	-2.9840u	-2.9840u
ibs	30.7773a	4.078e-22	4.078e-22
ibd	85.9470a	30.7765a	30.7765a
vgs	-715.7911m	-654.0502m	-654.0502m
vds	-419.8413m	-234.2089m	-234.2089m
vbs	234.2089m	0.	0.
vth	-583.3432m	-520.2438m	-520.2438m
vdsat	-161.4173m	-158.7329m	-158.7329m
vod	-132.4479m	-133.8064m	-133.8064m
beta	265.3957u	277.7935u	277.7935u
gam eff	555.4719m	557.0846m	557.0846m
gm	33.7945u	33.3259u	33.3259u
gds	390.8122n	991.9044n	991.9044n
gmb	8.8742u	9.7457u	9.7457u
cdtot	2.4432f	2.7716f	2.7716f
cgtot	6.7490f	6.8192f	6.8192f
cstot	8.1918f	8.5184f	8.5184f
cbtot	5.2388f	5.8816f	5.8816f
cgs	5.5812f	5.5856f	5.5856f
cgd	723.1107a	757.3319a	757.3319a

All transistors operate in saturation region.

```

****      small-signal transfer characteristics

v(vout)/vdiff      = 539.4155
input resistance at vdiff      = 1.000e+20
output resistance at v(vout)   = 11.1712x

```

Small signal transfer transfer characteristics



```

***** ac analysis tnom= 25.000 temp= 25.000 *****
gain_db= 54.6387      at= 1.0000
              from= 1.0000      to= 1.0000g
bandwidth= 7.0871k

```

### Ac analysis

```

**** voltage sources

subckt
element 0:vdiff      0:vb      0:vcm      0:vdd      0:vn      0:vp
volts    0.          450.0000m  900.0000m  1.8000    1.0000    850.0000m
current  0.          0.          0.          -5.9680u  0.          0.
power    0.          0.          0.          10.7424u  0.          0.

subckt
element 0:vss
volts    0.
current  5.9680u
power    0.

total voltage source power dissipation= 10.7424u      watts

```

### Power dissipation

Power hand calculation:  $1.8 \times 5.9680\mu = 10.7424\mu\text{W}$

### 3. Differential Mode

```

****      small-signal transfer characteristics

v(vout)/vdiff      = 539.4155
input resistance at      vdiff      = 1.000e+20
output resistance at v(vout)      = 11.1712x

```

Measured gain value: 539.4155(V/V)

gain calculation:

$$\begin{aligned}
 g_{m2}R_{out} &= -g_{m2} (g_{m4}r_{o4}r_{o2} \parallel g_{m6}r_{o6}r_{o8}), r_o = \frac{1}{g_{ds}} \\
 &= 52.8838 \mu \left( 57.9531 \mu \times \frac{1}{944.1758 n} \times \frac{1}{6.2814 \mu} \parallel 33.7945 \mu \times \frac{1}{390.8122 n} \times \frac{1}{991.9044 n} \right) \\
 &= 52.8838 \mu \times (9.7716 \times 10^6 \parallel 8.7178 \times 10^7) \\
 &= 52.8838 \mu \times 8.7866 \times 10^6 \cong 464.673 \text{ V/V}
 \end{aligned}$$

$$\text{Error} = \frac{464.673 - 539.4155}{539.4155} = -13.856\%$$

from .tf result:  $R_{out} = 11.1712 \text{ k}$ , and  $\text{gain} = g_{m2}R_{out}$

$$\therefore \text{gain} = 52.8838 \mu \times 11.1712 \text{ k} = 590.7755$$

$$\text{Error} = \frac{590.7755 - 539.4155}{539.4155} = 9.52\%$$

Hand calculation gain value

Reason of gain error:

- When using small signal parameters to calculate gain, I didn't consider body effect (body of NMOS/PMOS is connected to ground/vdd)
- When use  $R_{out}$  to calculate gain, we should use effective  $G_m$  to calculate gain value, because the current source( $M_b$ ) is not ideal which means it has a resistance.

4. Frequency Response/Pole and zero

```

*****
***** pole/zero analysis

input = 0:vdiff      output = v(vout)

      poles (rad/sec)                poles ( hertz)
real      imag      real      imag
-44.6363k    0.      -7.10408k    0.
-2.07008g   -1.63504g -329.464x   -260.225x
-2.07008g    1.63504g -329.464x   260.225x
-4.01821g    0.      -639.517x    0.
-4.42227g    0.      -703.826x    0.
-7.01161g    0.      -1.11593g    0.
-8.15773g    0.      -1.29834g    0.

      zeros (rad/sec)                zeros ( hertz)
real      imag      real      imag
-1.98363g   -3.15855g -315.705x   -502.698x
-1.98363g    3.15855g -315.705x   502.698x
-4.01801g    0.      -639.486x    0.
-4.42233g    0.      -703.836x    0.
-8.16157g    0.      -1.29895g    0.
52.3583g     0.      8.33308g     0.

```


Pole and zero

```

***** ac analysis tnom= 25.000 temp= 25.000 *****
gain_db= 54.6387      at= 1.0000
      from= 1.0000      to= 1.0000g
bandwidth= 7.0871k

```

Bandwidth: 7.0871kHz

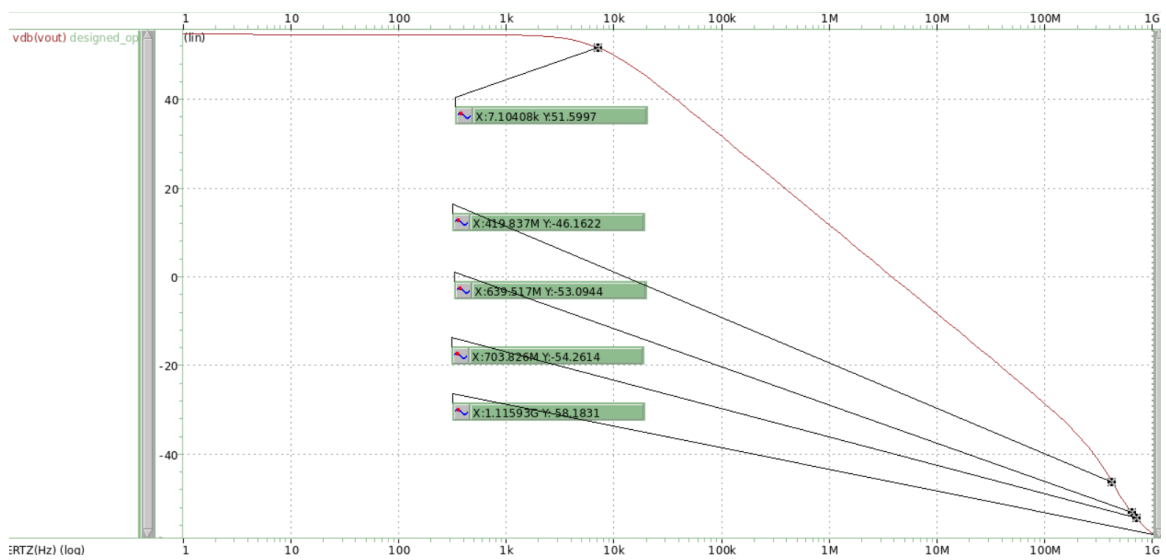

X axis: frequency (log (Hz)) – Y axis: open loop gain(dB)

Hand calculation of -3dB bandwidth (dominant pole):

$$\text{-3dB bandwidth} = \frac{1}{R_{out} * C_L} = \frac{1}{11.1712 \times 10^3 \cdot 2.7} = 44738 \text{ rad/s} = 7123.65 \text{ Hz}$$

$$\text{Error} = \frac{7123.65 - 7104.08}{7104.08} = 0.275 \%$$

\*Unit is MHz

Reason of bandwidth error:

- Although the first pole dominates the bandwidth value, the bandwidth is affected by all the poles. Therefore, if we only consider the first pole, there will be some errors.

## 5. Specification

Device size			
M1(W/L, m)	2um/0.5um	M5(W/L, m)	2um/0.5um
M2(W/L, m)	2um/0.5um	M6(W/L, m)	2um/0.5um
M3(W/L, m)	2.2um/0.5um	M7(W/L, m)	2um/0.5um
M4(W/L, m)	2.2um/0.5um	M9(W/L, m)	2um/0.5um
Mb(W/L, m)	6.8um/0.5um		

Table 1

total voltage source power dissipation= 10.7424u watts

Fig. 3 Power dissipation: 10.7424watts

```
***** ac analysis tnom= 25.000 temp= 25.000 *****
gain_db= 54.6387 at= 1.0000
from= 1.0000 to= 1.0000g
bandwidth= 7.0871k
```


Falt-band gain: 54.6387dB

## Part2
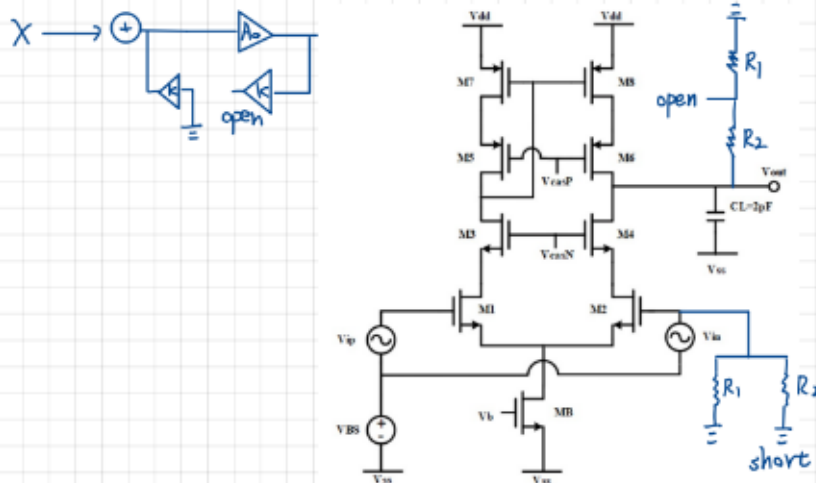
### 1. Discuss how I determine the value of R1 and R2

We need to consider the effect of feedback on I/O impedance:

It's an V-V amplifier, so we can break the ckt like this:



$$\text{gain} = \frac{g_{m2}(g_{m6}r_{o6}r_{o8} \parallel g_{m4}r_{o4}r_{o2} \parallel (R_1 + R_2))}{1 + g_{m2}(g_{m6}r_{o6}r_{o8} \parallel g_{m4}r_{o4}r_{o2} \parallel (R_1 + R_2)) \left( \frac{R_1}{R_1 + R_2} \right)}$$


so if  $R_1, R_2$  too small it will affect  $R_{out}$  and therefore decrease the gain.

$$\text{dominant pole} = \frac{1}{(g_{m6}r_{o6}r_{o8} \parallel g_{m4}r_{o4}r_{o2} \parallel (R_1 + R_2)) C_L}$$


so if  $R_1, R_2$  too large it will affect  $R_{out}$  and therefore decrease dominant pole value (bandwidth  $\downarrow$ )

$$\text{zero} = \frac{1}{C_n(R_n + (R_1 \parallel R_2))}$$

 so if  $R_1, R_2$  too large it will decrease the zero of mpnt node, so the graph will be like this



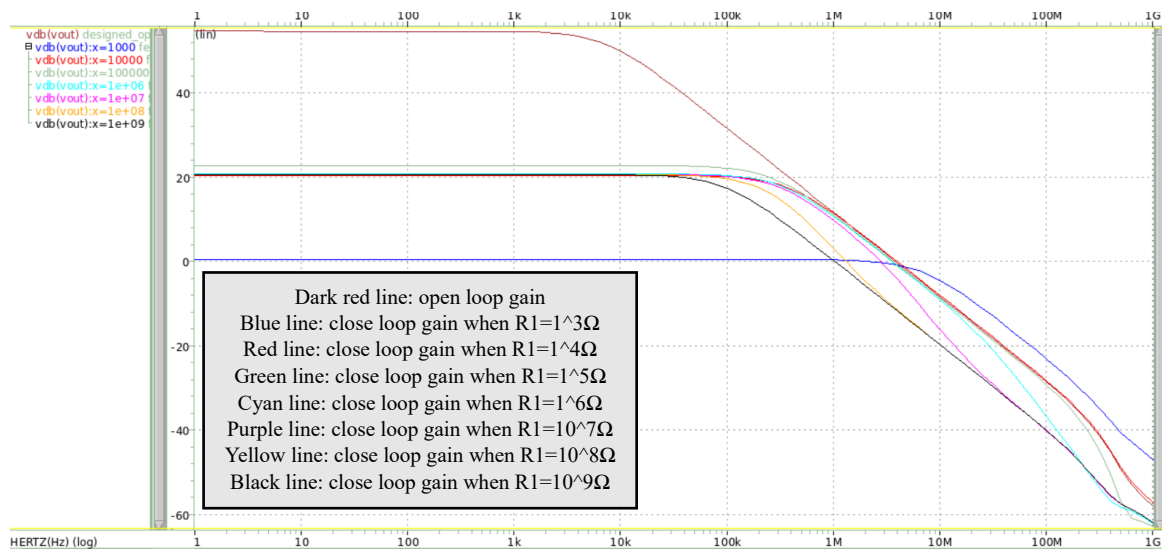So, to find proper  $r$  value I use dc sweep from  $1000\Omega$  to  $10^9\Omega$ , and we can see when  $r_1=10k\Omega$ , the graph is the most ideal.




X axis: frequency(log (Hz)) – Y axis: open loop gain(dB)

```

****      small-signal transfer characteristics

v(vout)/vdiff          = 10.4395
input resistance at    vdiff = 1.000e+20
output resistance at v(vout) = 207.5418k
  
```

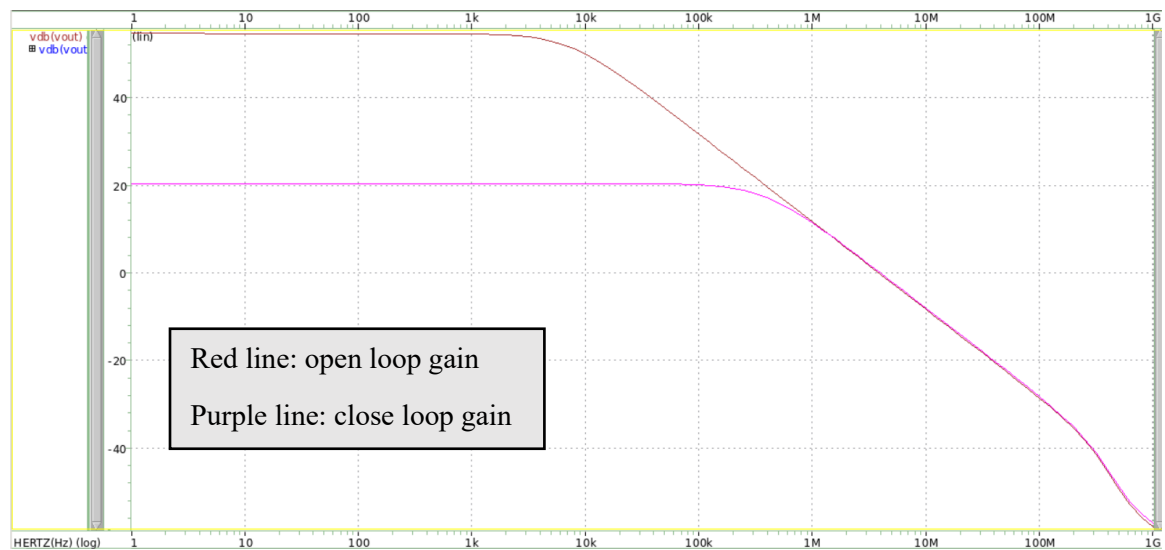But, when I look at the small-signal transfer characteristics, the gain doesn't achieve the speculation. Therefore, I sweep  $r1$  (9000  $\Omega$ , 9100  $\Omega$ , 9200  $\Omega$  ..... 11000 $\Omega$ ), then I found that when  $r1=9.8k \Omega$ ,  $r2=98k \Omega$ , the curve will be the most ideal and the gain is really close to 10(V/V).



X axis: frequency (log (Hz)) – Y axis: open loop gain(dB)


```

****      small-signal transfer characteristics

v(vout)/vdiff      = 10.0715
input resistance at      vdiff      = 1.000e+20
output resistance at v(vout)      = 199.8550k

```

 2. Observe the frequency response, you will see the gain change after we connect the feedback loop. Please mark the flat-band gain in both two curves and hand calculate the gain change, the flat-band gain after closed-loop as well as gain error.



X axis: frequency (log (Hz)) – Y axis: open loop gain(dB)

```

***** ac analysis tnom= 25.000 temp= 25.000 *****
gain_db= 54.6387      at= 1.0000
           from= 1.0000      to= 1.0000g
bandwidth= 7.0871k

```

Open loop flat-band gain: 54.6387dB

```


***** ac analysis tnom= 25.000 temp= 25.000 *****
*** parameter x = 1.0000k ***
gain_db= 20.0619      at= 1.0000
           from= 1.0000      to= 1.0000g
bandwidth= 395.6924k

```

Close loop flat-band gain: 20.0619dB

Hand calculation of gain:



 

$$\begin{aligned} V_{out} &= -A_o V_x \rightarrow V_x = \frac{-1}{A_o} V_{out} \\ \frac{V_x - V_m}{R_1} &= \frac{V_{out} - V_x}{R_2} \quad \dots (2) \\ \therefore \frac{-1/A_o V_{out} - V_m}{R_1} &= \frac{V_{out} - (-1/A_o V_{out})}{R_2} \end{aligned}$$

$$\rightarrow g_{am} = \frac{V_{out}}{V_m} = \frac{-1}{\frac{R_1}{R_2} + \frac{1}{A_o} (1 + \frac{R_1}{R_2})} \quad \therefore 9.8 \leq \frac{1}{\frac{R_1}{R_2} + \frac{1}{A_o} (1 + \frac{R_1}{R_2})} \leq 10.2$$

$$\therefore \frac{R_2}{R_1} = 19 \rightarrow \frac{R_1}{R_2} = 0.1, \quad A_o = 539,4155$$

$$\therefore g_{am} \approx -9.8002 \text{ (V/V)} = 19.8246 \text{ dB}$$



$$\text{gain change: } \frac{A_{\text{open loop}}}{A_{\text{close loop}}} = \frac{54.6387}{19.8246} = 2.7561$$

$$\text{error of flat-band gain: } \frac{19.8246 - 20.0619}{20.0619} = -1.18\%$$

Error reason:

The feedback loop will affect original opamp, but we didn't take it into consideration:

  It's an V-V amplifier, so we can break the ckt like this:



$$\text{gain: } \frac{g_{m2} (g_{m6} r_{o6} r_{o8} \parallel g_{m4} r_{o4} r_{o2} \parallel (R_1 + R_2))}{1 + g_{m2} (g_{m6} r_{o6} r_{o8} \parallel g_{m4} r_{o4} r_{o2} \parallel (R_1 + R_2)) \left( \frac{R_1}{R_1 + R_2} \right)}$$

so if  $R_1, R_2$  too small it will affect  $R_{out}$  and therefore decrease the gain.


3. Closed-loop gain is obviously lower than open-loop gain. Then, why do we need the feedback loop? How does it favor our needs?

- Gain desensitization against open loop gain variations due to process and temperature variations.

With feedback, the closed-loop gain relies less on the value of  $A_v$ . For example, in our circuit, the closed-loop gain is primarily determined by the ratio of  $r_1$  and  $r_2$ .

- Increase the bandwidth of the circuit.

 Although the gain decrease, the bandwidth of the circuit increase(tradeoff)



X axis: frequency (log (Hz)) – Y axis: open loop gain(dB)

- Insensitive to load variations.  
The negative feedback creates a more consistent output, so the load impedance will not affect the circuit.
- Improve the linearity of the circuit.  
The negative feedback reduces the common mode noise and also reduce the nonlinearities in the output signal.

4. Observe the frequency response. How does the dominant pole change after connecting feedback loop? And hand calculates the dominant pole after connecting feedback loop.

```

*****
*****  pole/zero analysis

input = 0:vdif          output = v(vout)

      poles (rad/sec)
real      imag
-44.6363k    0.
-2.07008g   -1.63504g
-2.07008g    1.63504g
-4.01821g    0.
-4.42227g    0.
-7.01161g    0.
-8.15773g    0.

      zeros (rad/sec)
real      imag
-1.98363g   -3.15855g
-1.98363g    3.15855g
-4.01801g    0.
-4.42233g    0.
-8.16157g    0.
52.3583g     0.

      poles ( hertz)
real      imag
-7.10408k    0.
-329.464x   -260.225x
-329.464x    260.225x
-639.517x    0.
-703.826x    0.
-1.11593g    0.
-1.29834g    0.

      zeros ( hertz)
real      imag
-315.705x   -502.698x
-315.705x    502.698x
-639.486x    0.
-703.836x    0.
-1.29895g    0.
8.33308g     0.

```

Dominant pole of open-loop: 7.10408kHz

```

***** pole/zero analysis

input = 0:vdif          output = v(vout)

      poles (rad/sec)          poles ( hertz)
real      imag      real      imag
-2.49224x    0.      -396.652k    0.
-2.07823g   -1.64084g -330.760x   -261.149x
-2.07823g    1.64084g -330.760x   261.149x
-4.07554g    0.      -648.643x    0.
-4.61715g    0.      -734.842x    0.
-6.78916g    0.      -1.08053g    0.
-8.24254g    0.      -1.31184g    0.
-20.2500g    0.      -3.22289g    0.

      zeros (rad/sec)         zeros ( hertz)
real      imag      real      imag
-1.92463g   -3.08556g -306.315x   -491.082x
-1.92463g    3.08556g -306.315x   491.082x
-4.06236g    0.      -646.544x    0.
-4.58028g    0.      -728.974x    0.
-8.31779g    0.      -1.32382g    0.
-17.5708g    0.      -2.79649g    0.
52.3609g     0.      8.33349g     0.

```

Dominant pole of open-loop: 396.652kHz

Hand calculation of dominant pole after connecting feedback loop.



bandwidth calculation:

$$\text{dominant pole of circuit} = \frac{1}{R_{out} * C_L} = \frac{1}{199855k \cdot 2p} = 2.5018M \text{ rad/s} = 398.375 \text{ kHz}$$

Error:  $\frac{398.375 - 393.6924}{393.6924} \approx 0.677\%$

Reason of error:

  It's an V-V amplifier, so we can break the clt like this:



dominant pole:  $\frac{1}{(g_{m6}r_{o6}r_{o8} \parallel g_{m4}r_{o4}r_{o2} \parallel (R_1 + R_2)) C_L}$

We can see when there is a feedback loop, dominant pole will be affected, and since we choose a proper  $R_1, R_2$ , the error is very small.

Summary table

Part1: open-loop simulation			
Working item	specification	simulation	calculation
Tail current	(uA)	5.968	-
Gain	>539(V/V)	539.4155	590.7755
Tial current bias	VBS(V)	0.45	-
Input common mode	Vb(V)	0.9	-
-3dB bandwidth	>7kHz	7.0871	7.12365
Power dissipation	uW	10.7424	10.7424
Part2: closed-loop simulation			
Working item	specification	simulation	calculation
Closed loop gain	10(V/V)	10.0715	9.8002