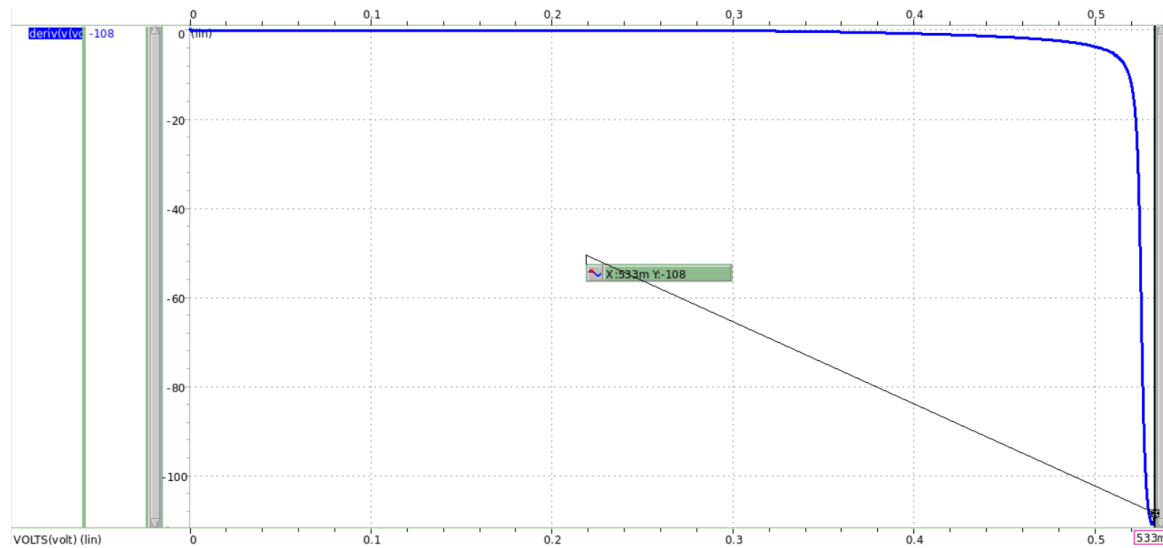


EE3225 Analog Integrated Circuit Analysis and Design HW3


110061217 王彦智

Part I-Cascade Amplifier

(a)



X axis: $V_{in}(V)$ – Y axis: Gain(V/V)

 

X axis: $V_{in}(V)$ – Y axis: $V_{out}(V)$

```

** 110061217 王彦智 hw3_a

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage

+0:vb1     = 900.0000m 0:vdd      = 1.8000  0:vin      = 533.0000m
+0:vout    = 499.4235m

**** voltage sources

subckt
element 0:vin      0:vb1      0:vdd
volts   533.0000m 900.0000m 1.8000
current 0.         0.         -5.1118u
power   0.         0.         9.2012u

total voltage source power dissipation= 9.2012u watts

```

Operating point and voltage source

- $V_{out} = 0.499V (0.5V \pm 10mv)$
- $|A_1| = 108V/V (>100V/V)$
- $V_{in} = 0.533V$
- $V_{b1} = 0.9V$
- $(\frac{W}{L})_{NMOS} = (\frac{W}{L})_{PMOS} = \frac{3\mu m}{3\mu m}$

How I design:

- Step1: designable parameters: V_{in} , V_{b1} , (W/L) of NMOS and PMOS
- Step2: gain should larger than 100:

$$\begin{aligned}
 |A_1| &= g_{mnmos}(r_{onmos} || r_{opmos}) \approx g_{mnmos} r_{opmos} \\
 &= \frac{2I_D}{V_{in} - V_{th}} * \frac{1}{\lambda_{pmos} I_D} = \frac{2}{(V_{in} - V_{th})\lambda_{pmos}} > 100V/V
 \end{aligned}$$

To increase gain, we should

1. Decrease V_{in} , and PMOS and NMOS should stay in saturation region (maintain I_d), so when decreasing V_{in} , we should also increase W/L of NMOS and PMOS. Also, we should consider if V_{in} is larger than V_{th} or not.
 2. Decrease λ_{pmos} by increasing L of PMOS.
- Step3: from step2, to have a large gain, I design $V_{in} \cong 0.55$, which is a little bit larger than V_{th} in this process. Also, from step2, W/L of NMOS and PMOS should be large enough and L also should be large enough to have a larger gain, so I design $W/L = 3\mu m/3\mu m$.

- Step4: Do .dc analysis to find Vb1 which make Vout = 0.5V. If there is no Vb1 that satisfy the condition, adjust Vin and do .dc analysis again. Finally, Vin = 0.533 and Vb1 = 0.9.
- Step5: check the result. Use .dc to check that gain is larger than 100. Use .op to check Vout = 0.5V and both NMOS and PMOS are in saturation region.

(b)

**** mosfets

```

subckt
element 0:mp      0:mn
model   0:p_18.1  0:n_18.1
region  Saturation Saturation
id      -5.1118u   5.1118u
ibs     6.208e-22 -1.008e-21
ibd     227.8188a -142.0151a
vgs     -900.0000m 533.0000m
vds     -1.3006   499.4235m
vbs     0.         0.
vth     -476.2435m 340.8760m
vdsat   -368.6683m 173.2277m
vod     -423.7565m 192.1240m
beta    64.6455u   302.0019u
gam_eff 557.0846m  507.4460m
gm       21.8546u   47.1123u
gds      52.5553n   392.3847n
gmb      7.1252u    9.2323u
cdtot    3.2640f    4.3769f
cgtot    57.5294f    59.9554f
cstot    65.6636f    63.1053f
cbtot    23.4601f    21.7777f
cgs      52.6225f    54.1463f
cgd      1.0851f     1.0554f

```

**** small-signal transfer characteristics

```

v(vout)/vin          = -105.8835
input resistance at   vin      = 1.000e+20
output resistance at v(vout) = 2.2476x

```

Gain and small signal parameters

Hand calculation: I connect gate of NMOS to ground and gate of PMOS to 1.8V, so we don't need to consider body effect.

$$|A_1| = g_{mnmos}(r_{onmos} || r_{opmos}) = g_{mnmos} \left(\frac{1}{g_{dsnmos}} || \frac{1}{g_{dspmos}} \right)$$

$$= \frac{g_{mnmos}}{g_{dsnmos} + g_{dspmos}} = \frac{47.1123u}{392.3847n + 52.5553n} = 105.8851$$

Check NMOS in saturation:

$$V_{gs} = 533mV > V_{th} = 340.8760mV$$

$$V_{gs} - V_{ds} = 533mV - 392.3847mV = 140.6153mV < V_{th} = 340.8760mV$$

Check PMOS in saturation:


$$|V_{gs}| = 900mV > |V_{th}| = 476.2435mV$$

$$|V_{gs} - V_{ds}| = 900mV - 1300.6mV = -400.6mV < V_{th} = 476.2435mV$$


Error:

$$\frac{105.8835 - 105.8851}{105.8851} = -1.5 * 10^{-3}\%$$


(c)

 

X axis: Vin(V) – Y axis: gain(V/V)

 

 X axis: $V_{in}(V)$ – Y axis: $V_{out}(V/V)$



X axis: $V_{b2}(V)$ – Y axis: $V_{out}(V)$

** 110061217 王彦智 hw3_b

```
***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node    =voltage    node    =voltage    node    =voltage
+0:vb2   = 1.0120  0:vdd    = 1.8000  0:vin    = 500.0000m
+0:vout  = 788.7143m
```

**** voltage sources

```
subckt
element 0:vin    0:vb2    0:vdd
volts   500.0000m 1.0120 1.8000
current 10.1129u  0.      -10.1129u
power   -5.0564u  0.      18.2031u
```

total voltage source power dissipation= 13.1467u watts

Operating point and voltage source

- $I_D = 10.1129\mu\text{A}$ (error: $\frac{10.1129 - 10}{10}10 = 1.11\% < 5\%$)
- $|A_2| = 17.7 \text{ V/V} (> 15\text{V/V})$
- $V_{in} = 0.5\text{V}$
- $V_{b2} = 1.012\text{V}$
- $V_{out} = 0.788\text{V}$
- $(\frac{W}{L})_{NMOS} = \frac{15\mu\text{m}}{1\mu\text{m}}$

How I design:

- Step1: designable parameters: V_{b2} , (W/L) of NMOS
- Step2: gain should larger than 15:

$$|A_2| = g_m(r_{onmos} || R_D) \approx g_m R_D = \frac{2I_D}{V_{gs} - V_{th}} * R_D = \frac{2}{(V_{b2} - V_{in} - V_{th})} > 15\text{V/V}$$

To increase gain, we should

1. Decrease V_{b2} , but NMOS should stay in saturation region, so when decreasing V_{b2} , we should also increase W/L of NMOS to maintain I_d .
 2. Decrease V_{th} by increasing L of NMOS, but it's not the main factor of the gain.
- Step3: from step2, to have a large gain, I design $V_{b2} \cong 1.05$, which is a little bit larger than $(V_{th} + V_{in} = 0.55 + 0.5)$. Also, W/L of NMOS should be large enough to maintain I_d , so I design $W/L = 15\mu\text{m}/1\mu\text{m}$.

- Step4: Do .dc analysis to find Vb2 which make $V_{out} = 0.8V(I_d = \frac{V_{dd}-V_{out}}{R_D} = \frac{1.8-V_{out}}{100k\Omega} = 10\mu A \rightarrow V_{out} = 0.8V)$. Finally, Vb2 = 1.012V. If there is not Vb2 that satisfy the condition, change W/L and do .dc analysis Vb2 again.
- Step5: check the result. Use .dc to check that gain is larger than 15. Use .op to check $I_d = 10\mu A$ and NMOS is in saturation region.

(d)

```
**** mosfets
```


```
subckt
element 0:mn
model 0:n_18.1
region Saturation
id 10.1129u
ibs -565.3016a
ibd -891.7188a
vgs 512.0000m
vds 288.7143m
vbs -500.0000m
vth 479.9309m
vdsat 81.5058m
vod 32.0691m
beta 4.7083m
gam eff 519.9006m
gm 196.1642u
gds 2.9998u
gmb 31.1424u
cdtot 19.7335f
cgtot 85.8967f
cstot 89.4453f
cbtot 48.2201f
cgs 70.5705f
cgd 5.3514f
```

```
**** small-signal transfer characteristics
```

```
v(vout)/vin = 17.7157
input resistance at vin = 5.6447k
output resistance at v(vout) = 76.9247k
```

Gain and small signal parameters

 Hand calculation: since I connected the body to ground, so I should consider body effect. Considering the following small signal model.



* there is no Rs in our circuit

By KCL at node of Vout: $-(g_m + g_{mb})V_{in} + (V_{out} - V_{in})/r_o + V_{out}/R_D = 0$

So

$$|A_2| = \frac{V_{out}}{V_{in}} = \frac{g_m + g_{mb} + \frac{1}{r_o}}{\frac{1}{r_o} + \frac{1}{R_D}} = \frac{196.1642\mu + 31.1424\mu + 2.9998\mu}{2.9998\mu + 1/100k} = 17.7160V/V$$

Check NMOS in saturation region:

$$V_{gs} = 512mV > V_{th} = 479.9309mV$$

$$V_{gs} - V_{ds} = 512mV - 223.2857mV = 140.6153mV < V_{th} = 479.9309mV$$

Error:

$$\frac{17.7157 - 17.7160}{17.7160} = -1.69 * 10^{-3}\%$$

(e)

i. yes.

- $V_X = 0.500635 \cong 0.5V$
- $V_{out} \text{ of (a) } = 0.4994235 \cong 0.5V$
- $V_{in} \text{ of (b) } = 0.5$

$$\text{Error: } \frac{0.500635 - 0.4994235}{0.4994235} = 0.24\%$$


```

** 110061217 王彦智 hw3_c

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
      node      =voltage      node      =voltage      node      =voltage
+0:vb1      = 900.0000m 0:vb2      = 1.0120  0:vdd      = 1.8000
+0:vin      = 533.0000m 0:vout     = 799.9460m 0:vx      = 500.6350m

```

Operating point

ii. No, overall gain doesn't equal $A_1 * A_2$.

```

****      small-signal transfer characteristics

```

```

      v(vout)/vin
      input resistance at      vin      = 1.000e+20
      output resistance at v(vout)      = 99.9431k

```

Overall gain

- $|A_1 * A_2| = 105.8835 * 17.7157 = 1875.8003 \text{ V/V}$
- $|A_{\text{cascade}}| = 4.6995 \text{ V/V}$

Why not equal: we neglect the input impedance and output impedance. That is, input impedance is not zero and output impedance is not infinite in this case.

Output impedance of common source amplifier (without considering body effect):

$$R_{\text{out}} = r_{\text{onmos}} || r_{\text{opmos}} = \frac{1}{g_{\text{dsnmos}} + g_{\text{dspmos}}} = \frac{1}{392.3847 \text{ n} + 52.5553 \text{ n}} = 2.2475 * 10^6 \Omega$$

Input impedance of common gate amplifier(considering body effect):

$$R_{\text{in}} = \frac{R_D + \frac{1}{g_{\text{ds}}}}{\frac{gm + g_{\text{mb}}}{g_{\text{ds}}} + 1}$$

$$= (100 \text{ k} + \frac{1}{2.9998 \text{ u}}) / (\frac{196.1642 \text{ u} + 31.1424 \text{ u}}{2.9998 \text{ u}} + 1) = 5645.667 \Omega$$

So, the overall gain should equal:

$$|A_{\text{cascade}}| = |A_1 * A_2| * \frac{R_{\text{in}}}{R_{\text{in}} + R_{\text{out}}}$$

$$= 1875.8003 * \frac{5645.667\Omega}{5645.667\Omega + 2247500\Omega} = 4.7001V/V$$

Error:

$$\frac{4.6995 - 4.7001}{4.7001} = 0.031\%$$

(f)

```

***** pole/zero analysis

input = 0:vin          output = v(vout)

      poles (rad/sec)          poles ( hertz)
real      imag      real      imag
-488.343x    0.      -77.7222x    0.
-2.46198g    0.      -391.837x    0.



      zeros (rad/sec)          zeros ( hertz)
real      imag      real      imag
33.2042g    0.       5.28462g    0.
597.299g    0.      95.0631g    0.


***** constant factor = 284.892u
*****
** 110061217 王彦智 hw3_c

***** ac analysis tnom= 25.000 temp= 25.000 *****
dcgain_in_db= 13.4411      at= 1.5849
              from= 1.0000      to= 100.0000g
bw= 74.7237x
ugb= 286.3280x

```


Pole/zero analysis and ac analysis

 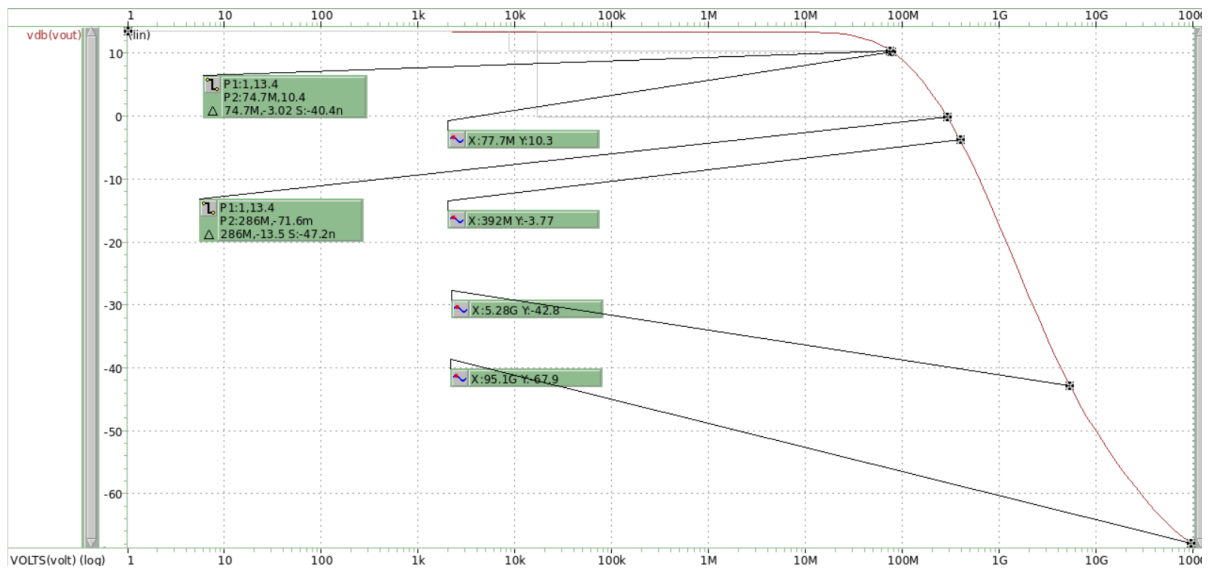

 

1st Zero: 2.28G; 2nd zero: 95.1G

 X axis: frequency(Hz) – Y axis: Vout(Vdb)



Unit-gain bandwidth: 392M; -3db bandwidth: 74.7M

X axis: frequency(Hz) – Y axis: Vout(Vdb)

(g)

Hand calculations:

**** small-signal transfer characteristics

$v(vout)/vin$ = -4.6995
 input resistance at vin = $1.000e+20$
 output resistance at $v(vout)$ = 99.9431k

Output resistance (Rout)

nodal capacitance table

node	=	cap	node	=	cap	node	=	cap
+0:vb1	=	57.5295f	0:vb2	=	85.5747f	0:vdd	=	89.1242f
+0:vin	=	59.9547f	0:vout	=	19.6828f	0:vx	=	96.7049f

Capacitance table: we can find Cout here

So, the dominant pole is:

$$\frac{1}{2\pi * R_{out} * C_{out}} = \frac{1}{2\pi * 99943.1\Omega * 19.6828fF} = 80.9469MHz$$

The definition of dominant pole is the pole with lowest frequency, so the dominant pole we measured is 77.7222MHz.

$$\text{Error: } \frac{77.7222-80.9469}{80.9469} = -3.983\%$$

Error is a little bit large, but acceptable. I think it is because we only consider the node of output, not every node of the circuit.

(h)

Table I Performance Table

Work item	Unit	Specification	Simulation	Calculation
Vdd	V	1.8		
Common Source Amplifier				
Vin	V	-	0.533	
Vb1	V	-	0.9	
Vo	V	0.5	0.4994235	
Gain(A ₁)	V/V	>100	105.8835	105.8851
Common Gate Amplifier				
Vin	V	0.5	0.5	
Vo	V	-	0.7887143	
I	μA	10	10.1129	
Gain(A ₂)	V/V	>15	17.7157	17.7160
Cascade Amplifier				
Vin	V	-	0.533	
Vx	V	0.5	0.500635	
Vo	V	-	0.7999460	
Gain(A ₁ *A ₂)	V/V	>1	4.6995	4.7001
Dominate Pole	MHz	>40	77.7222	80.9469
Unit Gain Bandwidth	MHz	>70	286.3280	