

Analog Integrated Circuit Analysis and Design I


Homework 2

110061217 王彦智

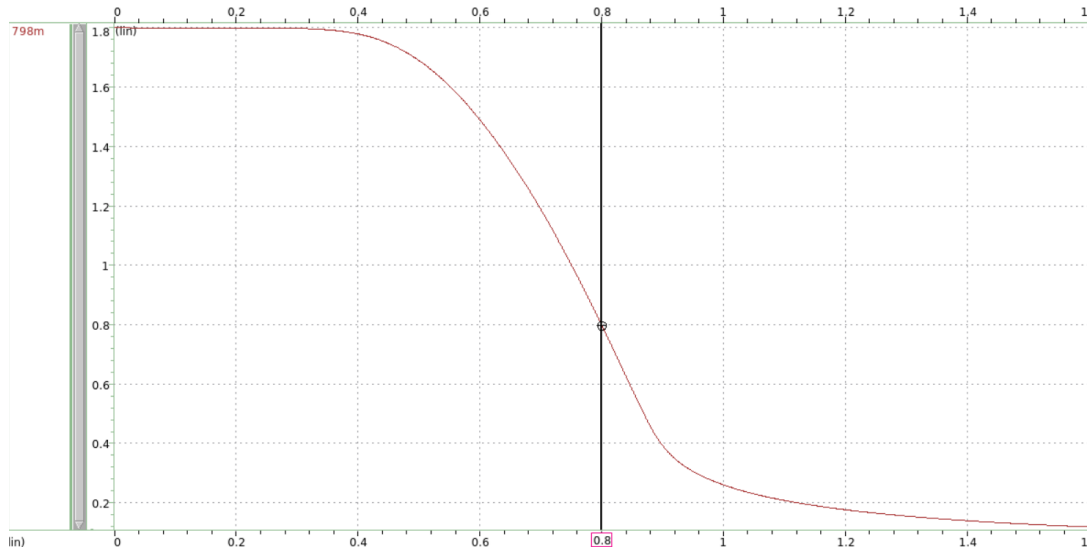
- Part 1

- DC sweep:

We can see when V_{in} is 0.8V, V_{out} is 0.798V(error: 0.25%) and the derivative of V_{out} is -4.25.



X axis: V_{in} (V)-Y axis: V_{out} (V)

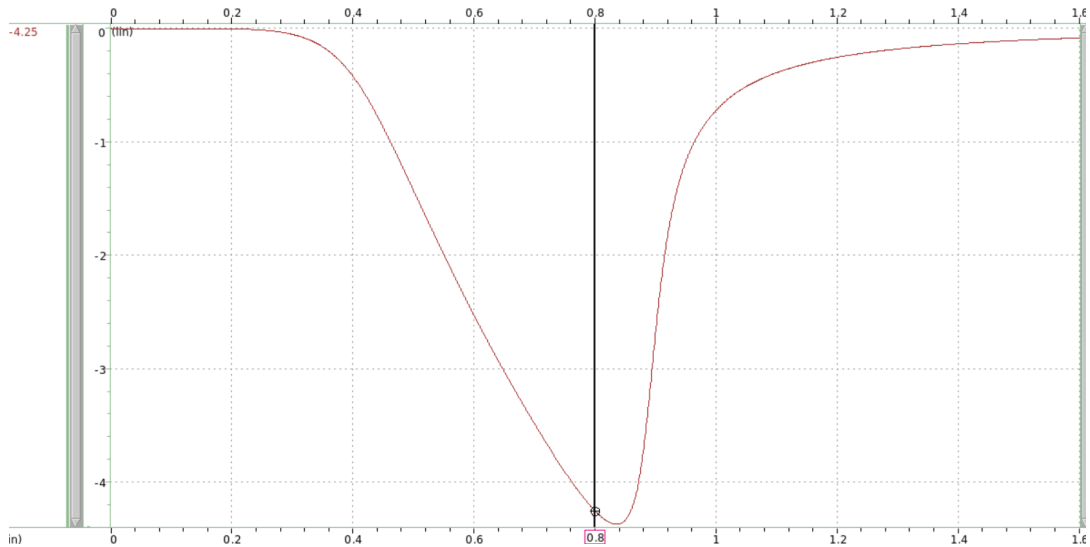

X axis: V_{in} (V)-Y axis: derivative of V_{out} (V)

- TF analysis

The following table is the TF analysis result, we can see A_v is -4.2563 when V_{in} is 0.8V. We can compare the result of DC sweep and TF analysis. In DC sweep, the meaning $\frac{\partial V_{out}}{\partial V_{in}}$ is “how V_{out} change when V_{in} change a little bit.” In TF analysis, we give some AC small signal on the DC operating point to see the output change. Therefore, the result of two analyses are basically the same, since the meaning of two operation are the same.

Vin(V)	Rin(Ω)	Rout(Ω)	$A_v(V/V)$
797.0000m	1.000e+20	43.8850k	-4.2394
798.0000m	1.000e+20	43.8627k	-4.2451
799.0000m	1.000e+20	43.8400k	-4.2507
800.0000m	1.000e+20	43.8168k	-4.2563
801.0000m	1.000e+20	43.7931k	-4.2617
802.0000m	1.000e+20	43.7689k	-4.2671
803.0000m	1.000e+20	43.7442k	-4.2724

TF Analysis

- Hand Calculation and Discussion

```

**info** dc convergence successful at Newton-Raphson method
1***** PrimeSim HSPICE -- R-2020.12-SP2 linux64 (May 24 2021 7074677) *****
*****
** 110061217 hw2 part1

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node    =voltage    node    =voltage    node    =voltage
+0:vdd   = 1.8000  0:vin    = 800.0000m  0:vout   = 798.3265m

**** voltage sources

subckt
element 0:vin    0:vdd
volts    800.0000m  1.8000
current  0.         -21.3122u
power    0.         38.3620u

total voltage source power dissipation= 38.3620u watts

**** resistors

subckt
element 0:rd
r value  47.0000k
v drop   1.0017
current  21.3122u
power    21.3479u

```

Operating point

```

subckt
element 0:mn
model 0:n_18.1
region Saturation
id 21.3122u
ibs -6.353e-21
ibd -114.4098a
vgs 800.0000m
vds 798.3265m
vbs 0.
vth 398.5086m
vdsat 332.9477m
vod 401.4914m
beta 308.1817u
gam_eff 507.4472m
gm 97.1615u
gds 1.5461u
gmb 18.3993u
cdtot 1.4212f
cgtot 6.8826f
cstot 7.8613f
cbtot 3.8609f
cgs 6.0654f
cgd 358.0754a

```

NMOS

Working item	SPEC	Your Design	Hand Calculation
V_{DD}	1.8V	1.8V	1.8V
$V_{in,DC}$	0.8V	0.8V	0.8V
$V_{out,DC}$	0.8V	798.3265mV	798.3266V
Gain A_V	>3.2(V/V)	4.2563(V/V)	4.2572(V/V)
R_D	<90k Ω	47k Ω	
I_D	<30uA	21.3122uA	
M_b W/L		1um/1um	

COMMON SOURCE PERFORMANCE TABLE

$$V_{out} = V_{DD} - I_d * R_D = 1.8 - 21.3122\mu A * 47k\Omega = 0.7983266V$$

$$Error = \frac{(0.7983265 - 0.7983266)}{0.7983266} * 100\% = -1.252 * 10^{-3}\%$$

$$A_V = \frac{\partial V_{out}}{\partial V_{in}} = -g_m R_D = -97.1615u \left(\frac{1}{\Omega} \right) * 47k\Omega = -4.5665(V/V)$$

$$Error = \frac{(4.2563 - 4.5665)}{4.5665} * 100\% = -7.28\%$$

$$R_{out} = (R_D \parallel \frac{1}{g_{ds}}) = (47K \parallel 646788.6941) = 43816.0334\Omega$$

$$Error = (43.8168 - 43.8160) / 43.8160 * 100\% = 0.0017\%$$

○ Discussion

▪ How I design the amplifier?

First, I choose $L = 1\mu\text{m}$, since it should not be too small, or it will have short-channel effect. Also, I don't want L to be too large, or it will waste the space of circuit. Second, I use a random W , L and R_D value to run hspice, I can get beta value($\frac{\text{beta}}{W/L} = u_n C_{ox}$), and V_{th} value. Third, I use $W/L = 1$, since $I_D = \frac{\frac{1}{2} \mu_n C_{ox} W}{L(V_{in} - V_{th})^2} < 30\mu\text{A}$. Then, I use $R_D = 50\text{k}\Omega$ to run hspice, and use $I_d = \frac{1}{2} * \frac{u_n C_{ox} W}{L} * (V_{gs} - V_{th})$ and $V_{out} = V_{DD} - I_d * R_D$ to find correct R_D . Finally, use new R_D to run hspice again, since I don't consider r_o , there will be some error, so I adjust it a little bit. The final R_D is $47\text{k}\Omega$.

first, set $L=1\mu$ and $\frac{W}{L}=1$, $R=50\text{k}$
 we can find $\text{beta} \cong 277.4\mu$, $V_{th} \cong 0.4\text{V}$
 $\rightarrow \therefore u_n C_{ox} = 277.4\mu / 1 = 277.4$
 $\begin{cases} I_d = \frac{1}{2} u_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})^2 \\ g_m = u_n C_{ox} \frac{W}{L} (V_{gs} - V_{th}) \end{cases}$
 $(I_d < 30\mu)$
 $I_d = \frac{1}{2} \times 277.4\mu \times \frac{W}{L} \times (0.4)^2 < 30\mu \dots \text{ok!}$
 $V_{DS} = V_{DD} - R \times I_d$
 $0.8 = 1.8 - R \times \frac{1}{2} \times 277.4\mu \times \frac{W}{L} \times (0.8 - 0.4)^2$
 $\therefore R \frac{W}{L} = \frac{1}{2.568 \times 10^{-5}} \cong 45\text{k}\Omega$
 $\rightarrow \text{choose } R=45\text{k}\Omega, \frac{W}{L}=1, L=1\mu (V_{th}=0.4\text{V})$
 代入後有誤差, 我認為是沒有考慮小 r_o ,
 微調後用 $R_d = 47\text{k}\Omega$ 最為接近

My calculation for design

- Why the hand calculation of A_V is different from the result?

I use the following formula to calculate the result:

$$V_{out} = V_{DD} - I_d * R_D = V_{DD} - \frac{1}{2} * u_n C_{ox} \frac{W}{L} * (V_{in} - V_{th})^2 * R_D$$

$$\rightarrow \frac{\partial V_{out}}{\partial V_{in}} = -u_n C_{ox} \frac{W}{L} * (V_{in} - V_{th}) * R_D$$

$$\text{And, when in saturation, } g_m = u_n C_{ox} \frac{W}{L} (V_{in} - V_{th})$$


$$\text{So, } A_V = \frac{\partial V_{out}}{\partial V_{in}} = -g_m R_D = -97.1615 \mu \left(\frac{1}{\Omega} \right) * 47k\Omega = -4.5665$$

However, by using small signal analysis, we should consider channel-length modulation effect, and by the following small signal module:

$$A_V = -g_m * R_{out} = -g_m * (R_D \parallel r_o)$$

$$= -97.1615 \mu \left(\frac{1}{\Omega} \right) \times 43.8168k\Omega = -4.2572 \left(\frac{V}{V} \right)$$
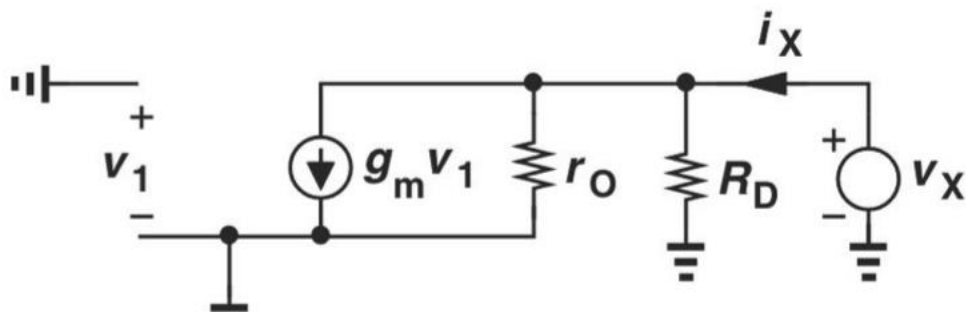
$$\text{Error can be reduce to } \frac{(4.2563 - 4.2572)}{4.2572} * 100\% = -0.0211\%$$




Small signal Model of Common Source Amplifier

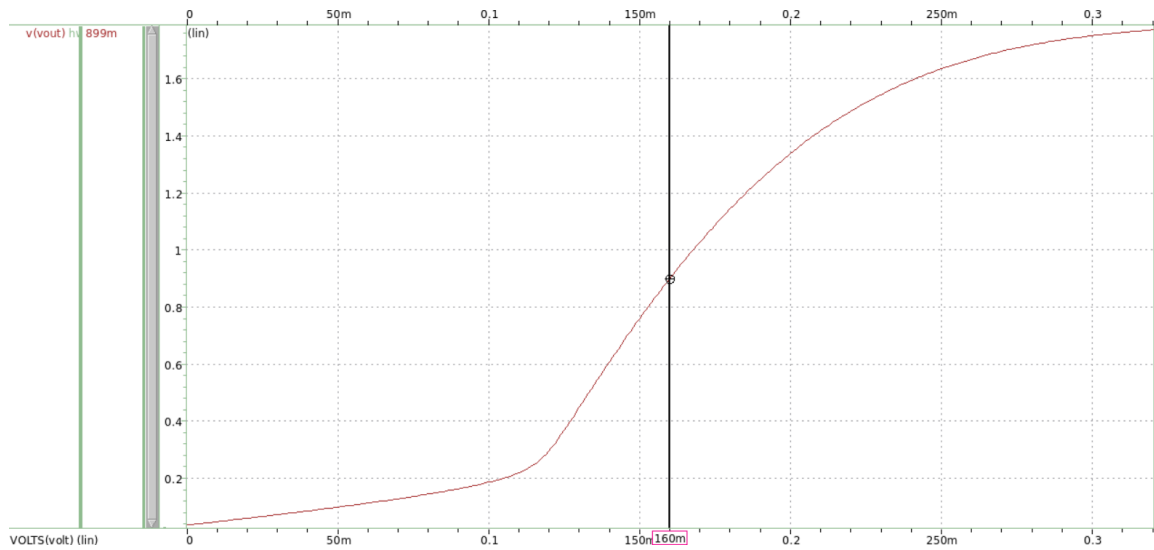
- Part 2

- DC sweep

We can see when V_{in} is 0.16V, V_{out} is 0.899V(error: 0.11%) and the derivative of V_{out} is 13.5.



X axis: V_{in} (V)-Y axis: V_{out} (V)

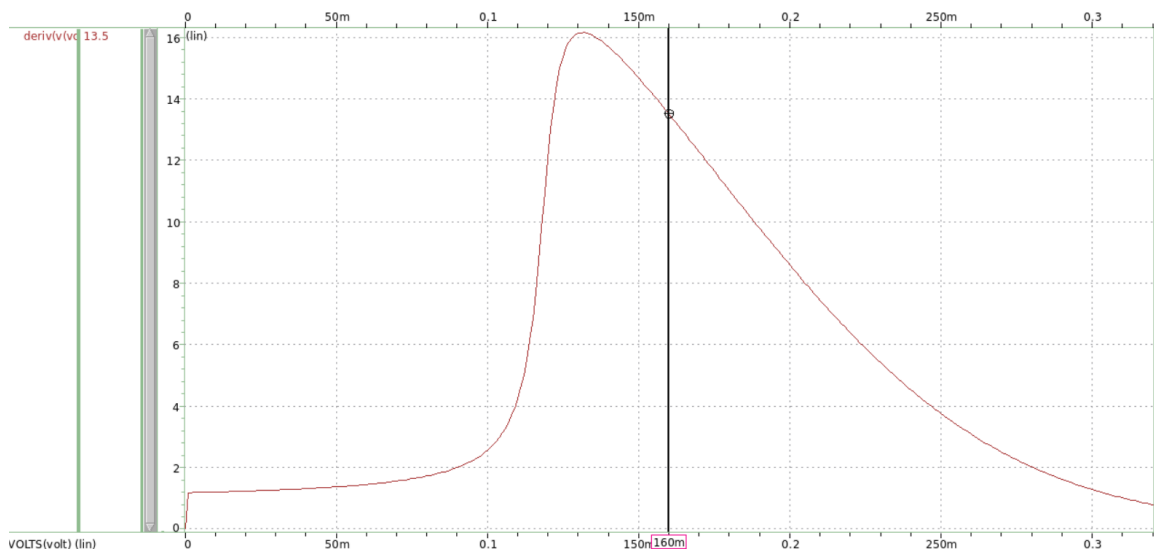

X axis: V_{in} (V)-Y axis: derivative of V_{out} (V)

- TF analysis

The following table is the TF analysis result, we can see A_v is 13.4464 when V_{in} is 0.16V. Comparing the result of DC sweep and TF analysis, we can see the result of two analyses are basically the same.

Vin(V)	Rin(Ω)	Rout(Ω)	Av(V/V)
155.0000m	5.1964k	61.9412k	14.0483
156.0000m	5.2408k	62.0637k	13.9293
157.0000m	5.2862k	62.1844k	13.8095
158.0000m	5.3327k	62.3034k	13.6891
159.0000m	5.3803k	62.4209k	13.5680
160.0000m	5.4290k	62.5370k	13.4464
161.0000m	5.4787k	62.6518k	13.3242
162.0000m	5.5296k	62.7654k	13.2016
163.0000m	5.5817k	62.8779k	13.0786
164.0000m	5.6348k	62.9893k	12.9552
165.0000m	5.6892k	63.0998k	12.8314

TF Analysis

- Hand Calculation

```

**info** dc convergence successful at Newton-Raphson method
1***** PrimeSim HSPICE -- R-2020.12-SP2 linux64 (May 24 2021 7074677) *****
*****
** 110061217 hw2 part2

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
node      =voltage      node      =voltage      node      =voltage

+0:vb      = 600.0000m 0:vdd      = 1.8000 0:vin      = 160.0000m
+0:vout     = 899.3692m

**** voltage sources

subckt
element 0:vin      0:vb      0:vdd
volts    160.0000m 600.0000m 1.8000
current  12.3374u  0.      -12.3374u
power    -1.9740u  0.      22.2073u

      total voltage source power dissipation= 20.2333u      watts

**** resistors

subckt
element 0:rd
r value  73.0000k
v drop   900.6308m
current  12.3374u
power    11.1115u

```

Operating point

**** mosfets

```

subckt
element 0:mn
model 0:n_18.1
region Saturation
id 12.3374u
ibs -1.965e-21
ibd -679.5079a
vgs 440.0000m
vds 739.3692m
vbs 0.
vth 383.9824m
vdsat 90.5847m
vod 56.0176m
beta 3.7299m
gam eff 507.4460m
gm 212.7323u
gds 2.2920u
gmb 43.5106u
cdtot 15.8434f
cgtot 76.5866f
cstot 84.6477f
cbtot 44.7636f
cgs 64.4158f
cgd 4.2951f

```

NMOS

Working item	SPEC	Your Design	Hand Calculation
V_{DD}	1.8V	1.8V	1.8V
$V_{in,DC}$	0.16V	0.16V	0.16V
$V_{out,DC}$	0.9V	899.3692mV	899.3698mV
Gain A_V	>10(V/V)	13.4464(V/V)	13.448 (V/V)
R_D	<90k Ω	73k Ω	
I_D	<30uA	13.3374uA	
V_b		0.6V	
M_b W/L		12um/1um	

COMMON GATE PERFORMANCE TABLE

$$V_{out} = V_{DD} - I_d * R_D = 1.8 - 12.3374\mu A * 73k\Omega = \mathbf{0.8993698V}$$

$$Error = \frac{899.3692 - 899.3698}{899.3698} * 100\% = -6.67 * 10^{(-4)}\%$$

$$A_V = \frac{\partial V_{out}}{\partial V_{in}} = g_m R_D = 212.7323u \left(\frac{1}{\Omega} \right) * 73k\Omega = \mathbf{15.5294(V/V)}$$

$$Error = \frac{13.4464 - 15.5294}{15.5294} * 100\% = -13.41\%$$

$$R_{out} = (R_D \parallel \frac{1}{g_{ds}}) = (73K \parallel 436300.1745) = \mathbf{62536.622\Omega}$$

$$Error = \frac{(62537 - 62536.622)}{62536.622} * 100\% = 2.5 * 10^{(-8)}\%$$

$$R_{in} = \frac{R_D + \frac{1}{g_{ds}}}{g_m r_o + 1} = \frac{73000 + 436300}{212.7323u * 436300 + 1} = 5428.763\Omega$$

$$\text{Error} = \frac{(5429 - 5428.763)}{5428.763} * 100\% = 0.00435\%$$

○ Discussion

▪ How I design the amplifier?

First, I choose $L = 1\mu m$, since it should not be too small, or it will have short-channel effect. Also, I don't want L to be too large, or it will waste the space of circuit. Second, I use a random W , L and R_D value to run hspice, I can get beta value ($\frac{\beta}{W/L} = u_n C_{ox}$), and V_{th} value. Third, to let NMOS operated in saturation region, $V_b > V_{th} + V_{in} \approx 0.56V$, I use $V_b = 0.6V$ to bias the NMOS. Third, since $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{th})^2 = \frac{1}{2} 400 \frac{W}{L} (0.04)^2 < 30\mu A$, and the required gain is large, so I use $W/L = 12$. Then, I use random R_D to run hspice, and use $I_d = \frac{1}{2} * \frac{u_n C_{ox} W}{L} * (V_{gs} - V_{th})^2$ and $V_{out} = V_{DD} - I_d * R_D$ to find correct R_D . Finally, use new R_D to run hspice again, since I don't consider r_o , there will be some error, so I adjust it a little bit. The final R_D is $73k\Omega$.

*I connect the source and body here since I don't want to have body effect.

*I choose $V_b = 0.6v$ since I don't want NMOS enter subthreshold region. Also, leg room can be lower (more space to operate).

▪ Why the hand calculation of A_V is different from the result?

I use the following formula to calculate the result:

$$V_{out} = V_{DD} - I_d * R_D = V_{DD} - \frac{1}{2} * u_n C_{ox} \frac{W}{L} * (V_b - V_{in} - V_{th})^2 * R_D$$

$$\rightarrow \frac{\partial V_{out}}{\partial V_{in}} = -u_n C_{ox} \frac{W}{L} * (V_b - V_{in} - V_{th}) * R_D$$


$$\text{And, when in saturation, } g_m = u_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{th})$$

$$\text{So, } A_V = \frac{\partial V_{out}}{\partial V_{in}} = g_m R_D = 212.7323u \left(\frac{1}{\Omega} \right) * 73k\Omega = 15.5294$$

However, by using small signal analysis, we should consider channel-length modulation effect and R_{in} (neglect g_{mb} here, since I connect body and source so V_{bs} is 0 here). By the following small signal module:

$$A_V = \frac{V_{out}}{V_{in}} = \frac{1+g_m r_o}{R_{in}(1+g_m r_o)} * R_D = 13.448(V/V)$$
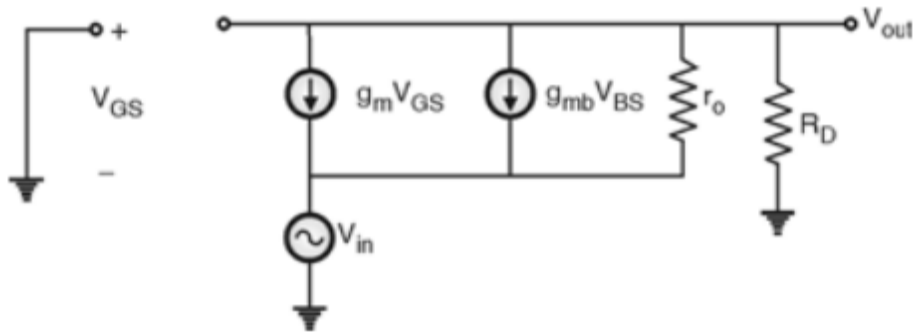
$$\text{Error can be reduce to } \frac{(13.4464 - 13.448)}{13.448} * 100\% = -6.5 * 10^{(-5)}\%$$




Small signal Model of Common Gate Amplifier

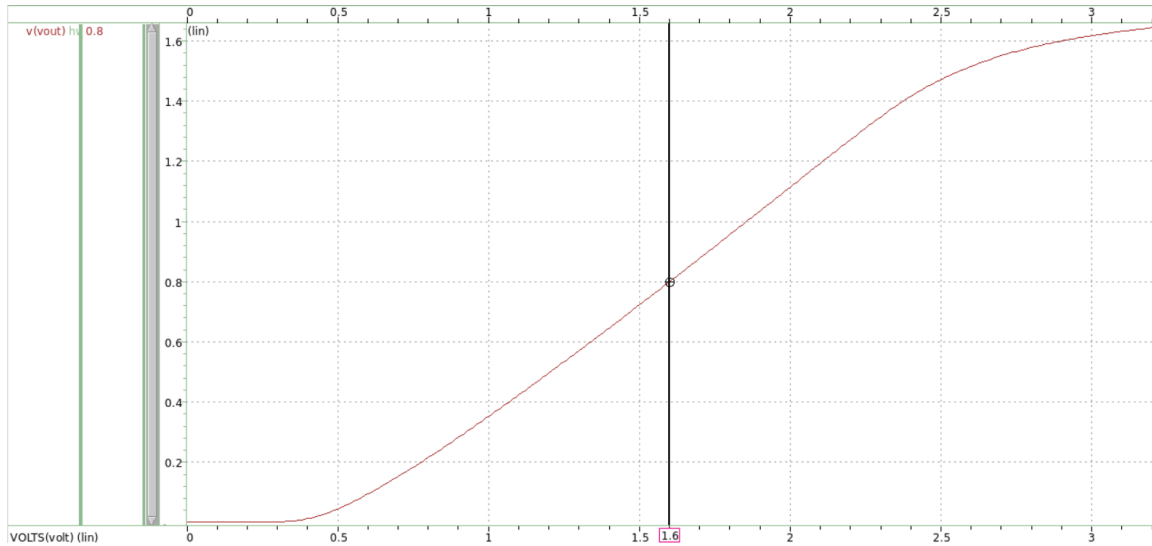
- Part 3

- DC sweep

We can see when V_{in} is 1.6V, V_{out} is 0.8V(error: almost 0%) and the derivative of V_{out} is 0.775.



X axis: $V_{in}(V)$ -Y axis: V_{out} (V)

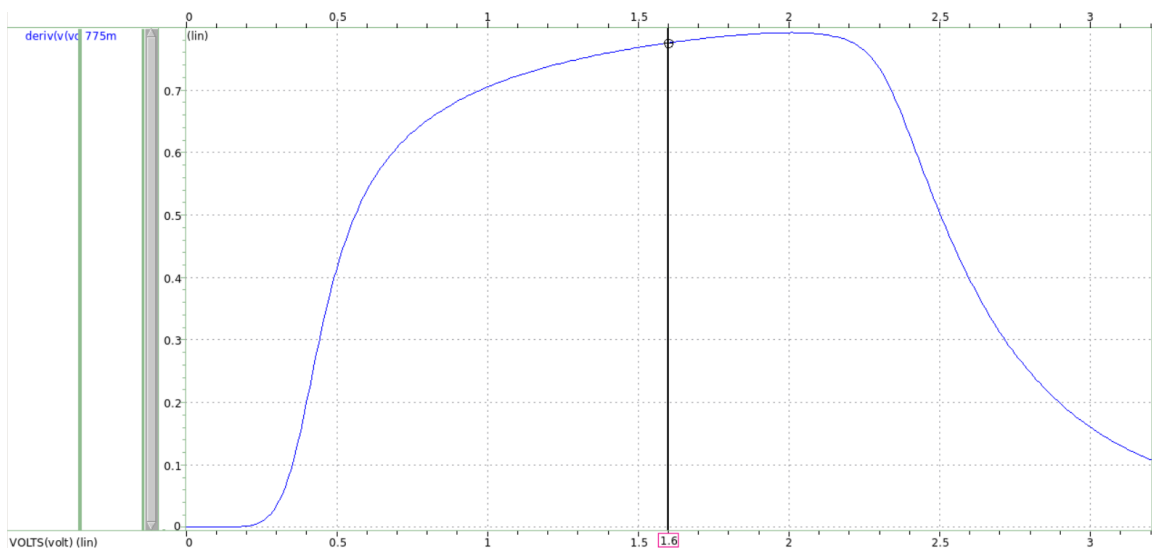

X axis: $V_{in}(V)$ -Y axis: derivative of V_{out} (V)

- TF analysis

The following table is the TF analysis result, we can see A_v is 0.7757681 when V_{in} is 1.6V. Comparing the result of DC sweep and TF analysis, we can see the result of two analyses are basically the same.

Vin(V)	Rin(Ω)	Rout(Ω)	Av(V/V)
1.5500	1.000e+20	8.0436k	772.2784m
1.5600	1.000e+20	8.0144k	772.9999m
1.5700	1.000e+20	7.9855k	773.7096m
1.5800	1.000e+20	7.9570k	774.4074m
1.5900	1.000e+20	7.9289k	775.0936m
1.6000	1.000e+20	7.9011k	775.7681m
1.6100	1.000e+20	7.8737k	776.4311m
1.6200	1.000e+20	7.8466k	777.0826m
1.6300	1.000e+20	7.8198k	777.7226m
1.6400	1.000e+20	7.7934k	778.3513m
1.6500	1.000e+20	7.7673k	778.9685m

TF Analysis

○ Hand Calculation

```

**info** dc convergence successful at Newton-Raphson method
1***** PrimeSim HSPICE -- R-2020.12-SP2 linux64 (May 24 2021 7074677) *****
*****
** 110061217 hw2 part3

***** operating point information tnom= 25.000 temp= 25.000 *****
***** operating point status is all simulation time is 0.
      node      =voltage      node      =voltage      node      =voltage
+0:vdd      = 1.8000 0:vin      = 1.6000 0:vout      = 799.8416m

**** voltage sources

subckt
element 0:vin      0:vdd
volts    1.6000    1.8000
current  0.        -21.6173u
power    0.        38.9112u

      total voltage source power dissipation= 38.9112u      watts

**** resistors

subckt
element 0:rs
r value  37.0000k
v drop   799.8416m
current  21.6173u
power    17.2905u

```

Operating point

**** mosfets

```

subckt
element 0:mn
model 0:n_18.1
region Saturation
id 21.6173u
ibs -6.444e-21
ibd -143.3363a
vgs 800.1584m
vds 1.0002
vbs 0.
vth 396.9768m
vdsat 334.1528m
vod 403.1816m
beta 308.2048u
gam eff 507.4472m
gm 98.2088u
gds 1.3530u
gmb 18.4990u
cdtot 1.3716f
cgtot 6.8796f
cstot 7.8579f
cbtot 3.8176f
cgs 6.0601f
cgd 355.4636a

```

NMOS

Working item	SPEC	Your Design	Hand Calculation
V_{DD}	1.8V	1.8V	1.8V
$V_{in,DC}$	1.6V	1.6V	1.6V
$V_{out,DC}$	0.8V	799.8416mV	799.8401mV
Gain A_V	>0.75(V/V)	775.7681m(V/V)	784.1909m(V/V)
R_s	<90k Ω	37k Ω	
I_D	<30uA	13.3374uA	
M_b W/L		1um/1um	

SOURCE FOLLOWER PERFORMANCE TABLE

$$V_{out} = I_d * R_s = 21.6173uA * 37k\Omega = 0.7998401V$$

$$\text{Error} = \frac{(799.8416 - 799.8401)}{799.8401} * 100\% = 1.8753 * 10^{(-4)}\%$$

$$A_V = \frac{\partial V_{out}}{\partial V_{in}} = \frac{g_m R_s}{1 + g_m R_s} = \frac{37K\Omega}{1 + 98.2088u * 37K\Omega} = 0.7984935(V/V)$$

$$\text{Error} = \frac{(799.8416 - 798.4935)}{798.4935} * 100\% = 0.16\%$$

$$R_{out} = \frac{1}{g_m} || R_s = \frac{1}{98.2088u + \frac{1}{37k}} = 8386.741\Omega$$

$$\text{Error} = \frac{(7901 - 8386.741)}{8386.741} * 100\% = -6.1384\%$$

○ Discussion

▪ How I design the amplifier?

First, I choose $L = 1\mu\text{m}$, since it should not be too small, or it will have short-channel effect. Also, I don't want L to be too large, or it will waste the space of circuit. Second, I use a random W , L and R_D value to run hspice, I can get beta value ($\frac{\beta}{W/L} = u_n C_{ox}$), and V_{th} value. Third, since $I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{th})^2 < 30\mu\text{A}$, and the required gain is not large, so I use $W/L = 1$. Then, I use random R_D to run hspice, and use $I_d = \frac{1}{2} * \frac{u_n C_{ox} W}{L} * (V_{gs} - V_{th})$ and $V_{out} = I_d * R_S$ to find correct R_S . Finally, use new R_S to run hspice again, since I don't consider r_o , there will be some error, so I adjust it a little bit. The final R_D is $37\text{k}\Omega$.


*I connect the body and source here since I don't want to have body effect.

▪ Why the hand calculation of R_{out} is different from the result?

We should also consider R_S in the circuit (channel length modulation), so by the following circuit which is in the course materials:

$$R_{out} = \frac{1}{g_m} || r_o || R_S = \frac{1}{\frac{1}{98.2088\mu} + \frac{1}{1.3530\mu} + \frac{1}{37000}} = 7899.4\Omega$$
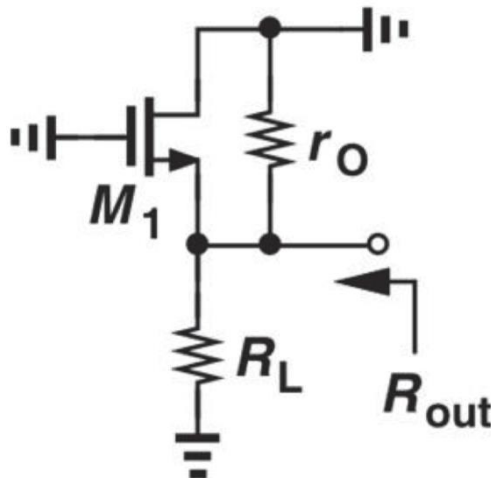
$$\text{Error can be reduce to } \frac{(7901 - 7899.4)}{7899.4} * 100\% = 0.0205\%$$



Source follower output impedance