

EE3235 Analog Integrated Circuit Analysis and design I


Homework 4

Ideal OP circuit

110061217 王彦智

1. Unity-gain Amplifier

(a) DC Sweep

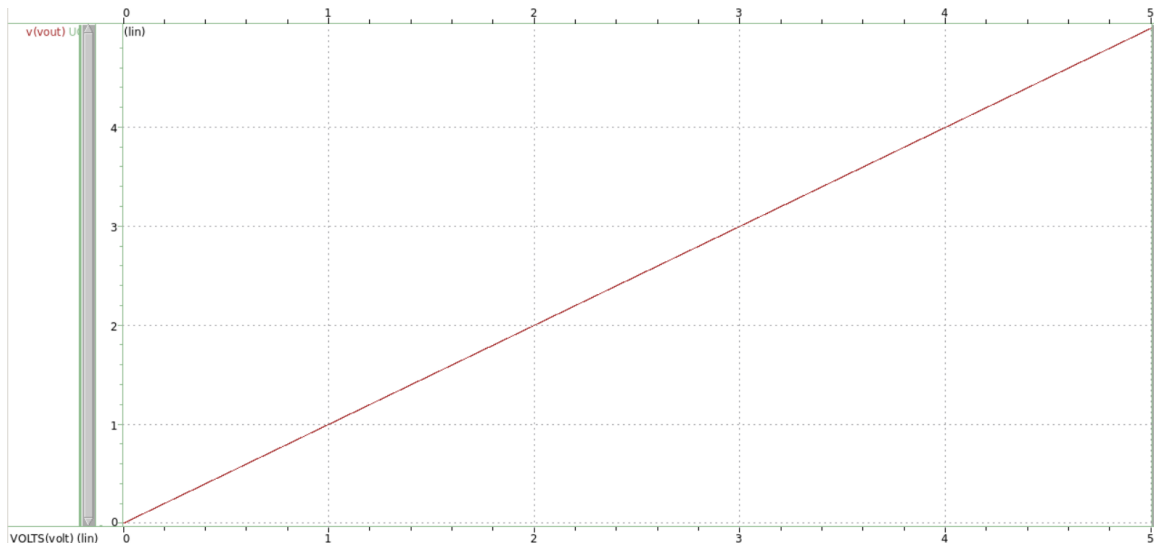

X axis: Vin(V) – Y axis: Vout(V)

```
$DATA1 SOURCE='PrimeSim HSPICE' VERSION='R-2020.12-SP2 linux64' PARAM_COUNT=0
.TITLE '** 110061217 王彦智 hw4_1'
derivative_of_vout temper alter#
0.9990 25.0000 1
```

Derivative of Vout when Vin is 2.5V: 0.9990(V/V)


(b) TF Analysis

**** small-signal transfer characteristics

```
v(vout)/vin = 999.0010m
input resistance at vin = 1.000e+20
output resistance at v(vout) = 0.
```

TF Analysis

Calculation of DC gain:

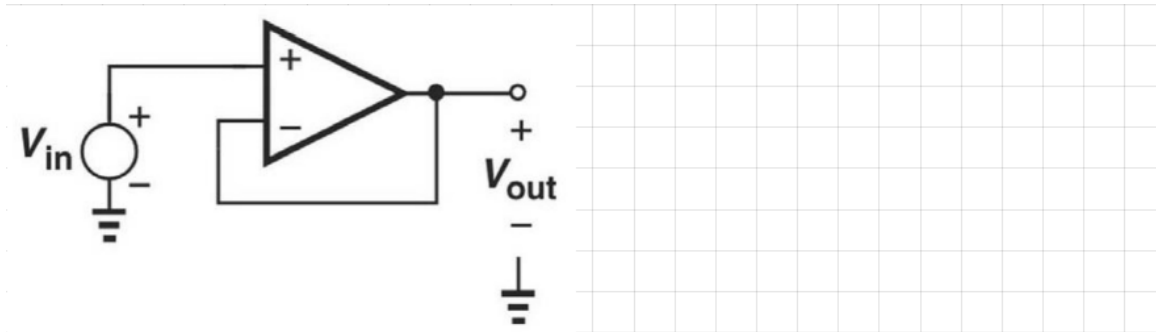

$$V_{out} = (V_{in} - V_{out}) \times A_o$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{A_o}{A_o + 1}$$

$$\rightarrow A_o = 60 \text{ dB} = 1000$$


$$\therefore \text{DC gain} = \frac{V_{out}}{V_{in}} = \frac{1000}{1001} \approx 999.000999 \text{ m (V/V)} \#$$

Error:

$$\frac{999.001 - 999.0009}{999.0009} = 10^{-5}\%$$

2. Noninverting Amplifier

(a) DC Sweep

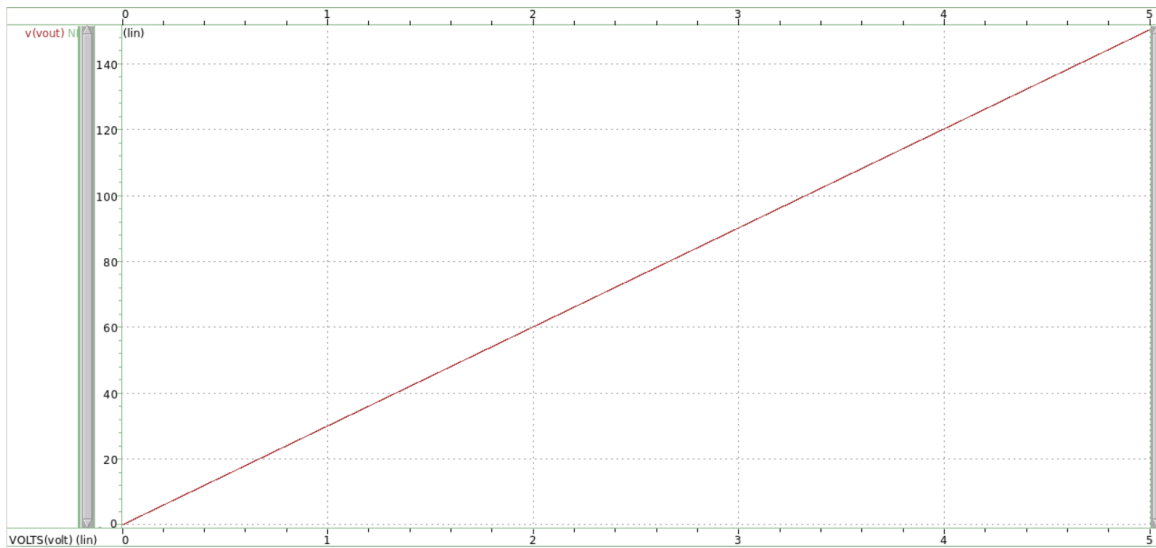

X axis: Vin(V) – Y axis: Vout(V)

```

$DATA1 SOURCE='PrimeSim HSPICE' VERSION='R-2020.12-SP2 linux64' PARAM_COUNT=0
.TITLE '** 110061217 王彦智 hw4_2'
derivative_of_vout temper alter#
30.0679 25.0000 1

```

Derivative of Vout when Vin is 2.5V: 30.0679(V/V)

(b) TF Analysis

**** small-signal transfer characteristics


```

v(vout)/vin          = 30.0679
input resistance at   vin      = 1.000e+20
output resistance at v(vout)   = 0.

```

TF Analysis

Calculation of DC gain:

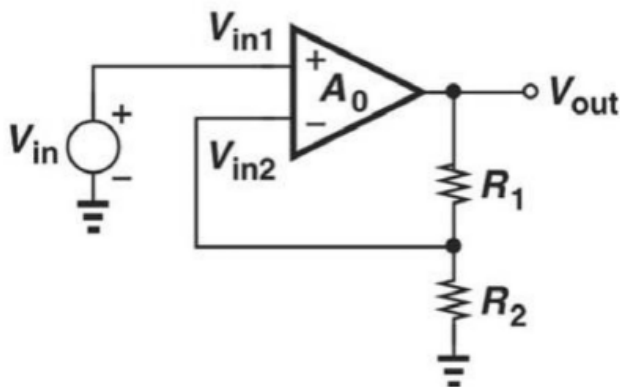

$$V_{out} = (V_{in} - V_{in2}) A_0$$

$$V_{in2} = \frac{R_2}{R_1 + R_2} V_{out}$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{A_0}{1 + \frac{R_2}{R_1 + R_2} A_0}$$

$$\rightarrow A_0 = 1000, R_1 = 30k\Omega, R_2 = 1k\Omega$$

$$\therefore \text{DC gain} = \frac{V_{out}}{V_{in}} = 30.067895 \text{ (V/V)} \quad \#$$

Error:

$$\frac{30.0679 - 30.097895}{30.0679} = 1.6 * 10^{-5}\%$$

(c) How do you design your circuit to meet the SPEC? Describe your design considerations.

$$\frac{V_{out}}{V_{in}} \approx \left(1 + \frac{R_1}{R_2}\right) \left(1 - \left(1 + \frac{R_1}{R_2}\right) \frac{1}{1000}\right) = 30$$

$$\hat{=} R_1/R_2 = x$$

$$\rightarrow (x+1) \left(1 - (1+x)/1000\right) = 30$$

$$(x+1) (1000 - (1+x)) = -30000$$

$$x^2 - 998x - 999 = -30000$$

$$x^2 - 998x + 29001 = 0$$

$$\therefore x = \frac{998 \pm \sqrt{998^2 - 4 \times 29001}}{2} \rightarrow x = \frac{29.9584 \text{ or } 968.0415}{2}$$


$$\therefore \text{choose } \frac{R_1}{R_2} = 29.9584 \approx 30 \quad \text{gain error too large}$$

$$\therefore \text{choose } R_1 = 30k\Omega, R_2 = 1k\Omega$$

$$\text{error} = \frac{30.0979 - 30}{30} = 0.226\% < 1\% \checkmark$$

3. Inverting Amplifier

(a) DC Sweep

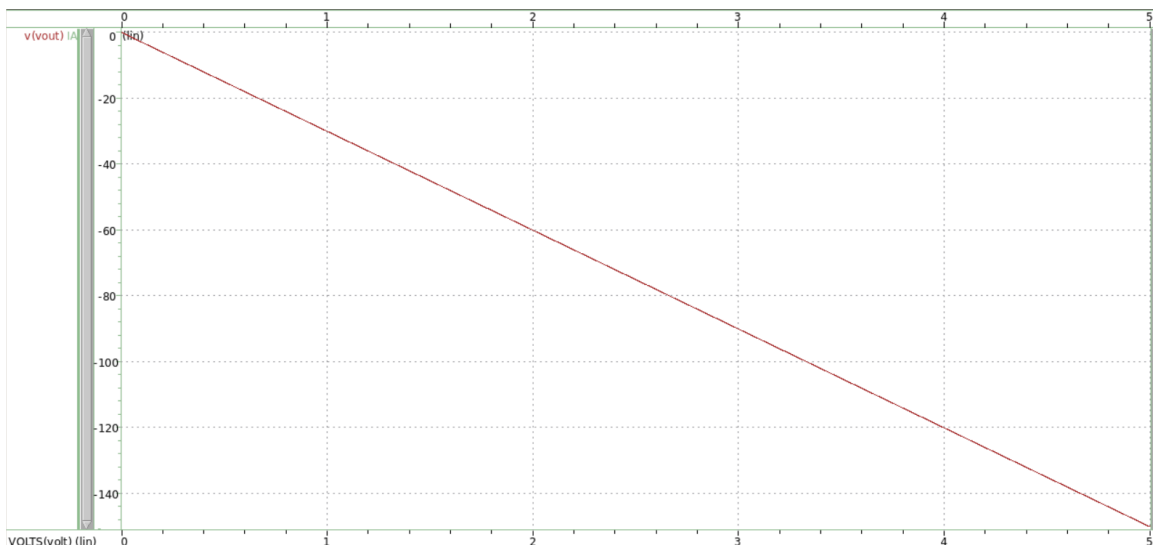

X axis: Vin(V) – Y axis: Vout(V)

```
$DATA1 SOURCE='PrimeSim HSPICE' VERSION='R-2020.12-SP2 linux64' PARAM_COUNT=0
.TITLE '** 110061217 王彦智 hw4_3'
derivative_of_vout temper alter#
-30.0388 25.0000 1
```

Derivative of Vout when Vin is 2.5V: -30.0388(V/V)


(b) TF Analysis

**** small-signal transfer characteristics

```
v(vout)/vin = -30.0388
input resistance at vin = 1.0310k
output resistance at v(vout) = 0.
```

TF Analysis

Calculation of DC gain:

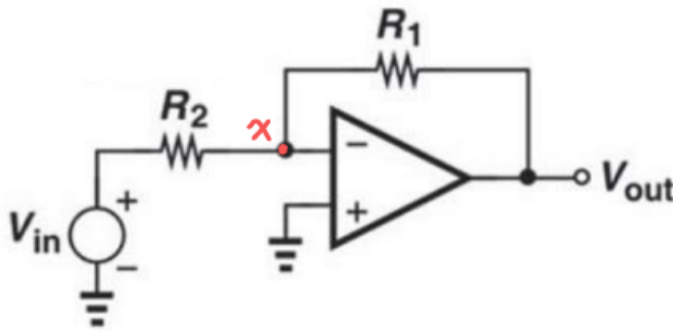

$$\begin{cases} \frac{V_m - V_x}{R_2} = \frac{V_x - V_{out}}{R_1} \\ V_{out} = (V_{m1} - V_{m2}) A_o = V_x A_o \end{cases}$$

$$\therefore \frac{V_{out}}{V_m} = - \frac{1}{\frac{R_2}{R_1} + \frac{1}{A_o} \left(1 + \frac{R_2}{R_1}\right)}$$

$$\rightarrow A_o = 1000, R_2 = 1k\Omega, R_1 = 31k\Omega$$

$$\therefore \text{Ac gain} = \frac{V_{out}}{V_m} = -30.038759 \text{ (V/V)} \quad \#$$

Error:

$$\frac{30.0388 - 30.038759}{30.038759} = 1.36 \times 10^{-4}\%$$

(c) How do you design your circuit to meet the SPEC? Describe your design considerations.

$$\frac{V_{out}}{V_{in}} \approx -\frac{R_1}{R_2} \left(1 - \frac{1}{A_0} \left(1 + \frac{R_1}{R_2} \right) \right) = -30$$

$$\triangleq R_1/R_2 = X$$

$$-X \left(1 - \frac{1}{1000} (1 + X) \right) = -30$$

$$\therefore X (1000 - (1 + X)) = 30$$

$$\therefore 999X - X^2 = 30000 \rightarrow X^2 - 999X + 30000 = 0$$

$$\therefore X = \frac{999 \pm \sqrt{999^2 - 4 \times 30000}}{2} = 30.99146 \text{ or } 968.0085$$

gain error too large


$$\rightarrow \text{choose } \frac{R_1}{R_2} = 30.99146 \approx 31$$

$$\rightarrow \text{choose } R_1 = 31 \text{ k}\Omega, R_2 = 1 \text{ k}\Omega$$

$$\text{error: } \frac{30.038759 - 30}{30} \approx 0.129\% < 1\% \quad \checkmark$$

4. Voltage Adder + Integrator

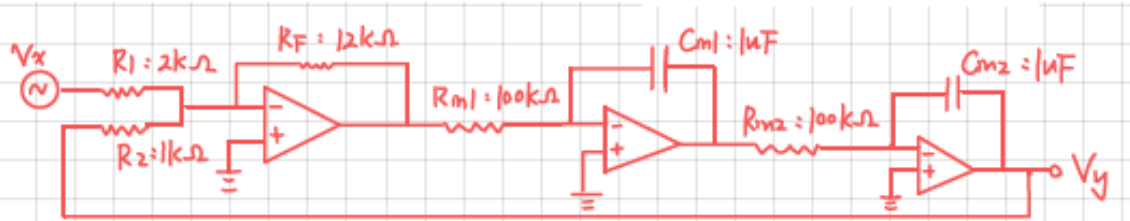(a) Describe your design consideration and show the schematic.



$$\begin{aligned}
 V_y(t) &= \int \left(\int -600 V_x(t) - 1200 V_y(t) dt \right) dt \\
 &= -10 \int \left(-10 \int (-6 V_x(t) - 12 V_y(t) dt \right) dt \\
 \text{let } -6 V_x(t) - 12 V_y(t) &= V_{out0}
 \end{aligned}$$

1. One Voltage Adder:

$$\rightarrow V_{out0} = -R_F \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} \right) = -6 V_x(t) - 12 V_y(t)$$

$$\text{let } V_1 = V_x(t) \quad V_2 = V_y(t)$$

$$\therefore \text{choose } R_F = 12k\Omega, R_1 = 2k\Omega, R_2 = 1k\Omega \quad \#$$

$$\text{let } V_{out1} = -10 \int V_{out0} dt$$

2. first integrator:

$$V_{out1} = \frac{-1}{RC} \int V_{in} dt = -10 \int V_{out0} dt$$

$$\text{let } V_{in} = V_{out0} \rightarrow \frac{-1}{RC} = -10$$

$$\therefore \text{choose } R = 100k, C = 1\mu F \quad \#$$

3. second integrator:

$$V_y = \frac{-1}{RC} \int V_{in} dt = -10 \int V_{out1} dt$$

$$\text{let } V_{in} = V_{out1} \rightarrow \frac{-1}{RC} = -10$$

$$\therefore \text{choose } R = 100k, C = 1\mu F \quad \#$$

(b) Suppose all initial conditions are 0 and $V_x(t)$ is an unit step input. Please do hand calculation to find the transient response of $V_y(t)$ and the period of the waveform at $V_y(t)$.

$$V_y(t) = \int \left(\int -600 V_x(t) - 1200 V_y(t) dt \right) dt$$

→ Laplace transform

$$\overline{V_y}(s) = \frac{1}{s^2} (-600 \overline{V_x}(s) - 1200 \overline{V_y}(s))$$

$$s^2 \overline{V_y}(s) = -600 \overline{V_x}(s) - 1200 \overline{V_y}(s)$$

$$(s^2 + 1200) \overline{V_y}(s) = -600 \overline{V_x}(s)$$

$$\therefore \overline{V_x}(s) = \mathcal{L}\{V_x(t) = u(t)\} = \frac{1}{s}$$


$$\therefore \overline{V_y}(s) = \frac{-600}{s^2 + 1200} \times \frac{1}{s} = \frac{1}{2} \left(\frac{s}{s^2 + 1200} - \frac{1}{s} \right)$$

$$\therefore \mathcal{L}^{-1}\left(\frac{\overline{V_y}(s)}{\overline{V_x}(s)}\right) = \frac{1}{2} (\cos(20\sqrt{3}t) - u(t))$$

$$\text{period: } \cos(20\sqrt{3}(t+T)) = \cos(20\sqrt{3}t)$$

$$\therefore 20\sqrt{3}T = 2\pi \quad T = \frac{2\pi}{20\sqrt{3}} \approx 0.181379 \text{ s}$$

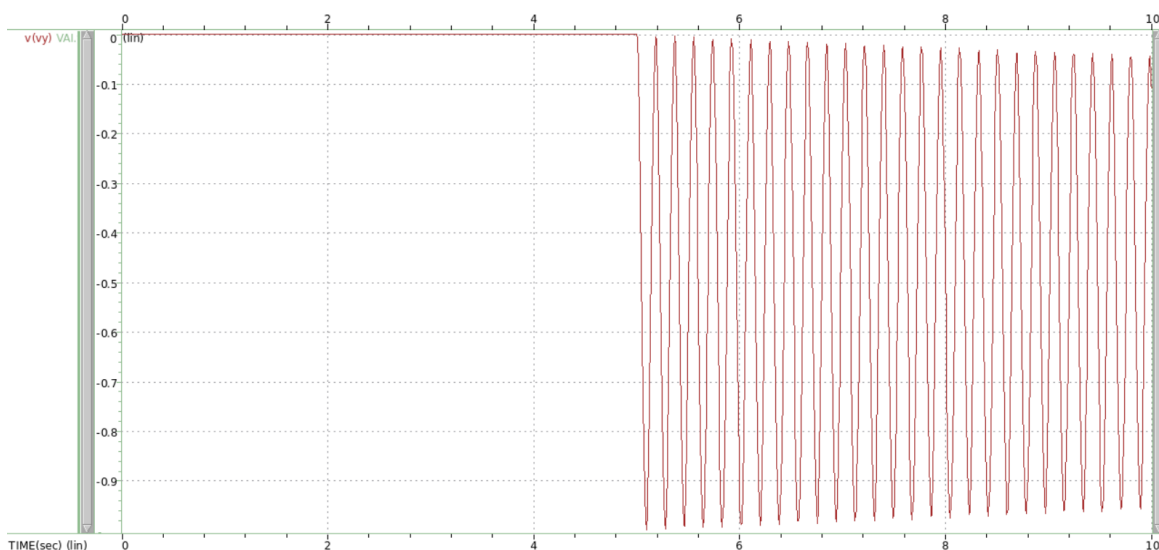(c) Let $V_x(t)$ be a unit step input. Plot the transient response of $V_y(t)$ and measure the period of $V_y(t)$.




transient response of $V_y(t)$: X axis: t – Y axis: $V_y(t)$

```
$DATA1 SOURCE='PrimeSim HSPICE' VERSION='R-2020.12-SP2 linux64' PARAM_COUNT=0
.TITLE '** 110061217 王彦智 hw4_4'
vmin1          vmin2          tp          temper
alter#
1 -0.9994      -0.9566        4.8019      25.0000
```

Period of the waveform

Calculation of period that I measured:

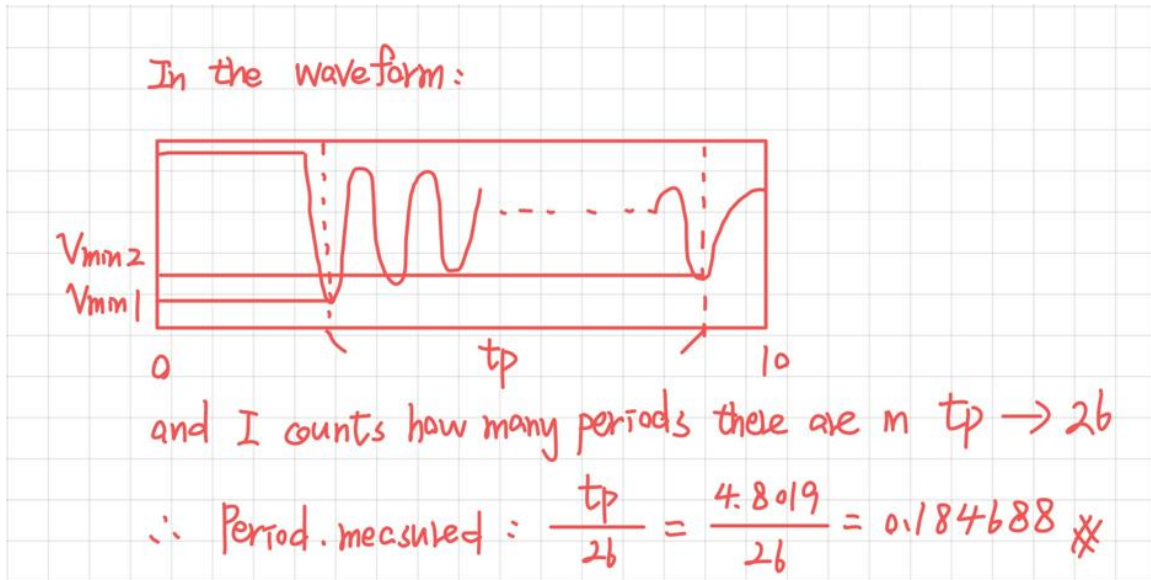


(d) What is the error between calculated waveform period and the simulation waveform period?

$$\frac{0.184688 - 0.181379}{0.181379} = 1.824\%$$

Error is 1.824%. I think it is because I didn't consider finite gain when I design, and if we consider finite gain:

1. Period will be different since the relationship between input and output is different.
2. The waveform is not sin function but sin function with damping (like the simulated result).

* Consider finite gain:
1. Voltage Adder

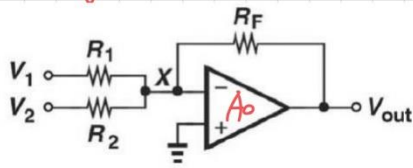

$$\frac{V_1 - V_X}{R_1} + \frac{V_2 - V_X}{R_2} = \frac{V_X - V_{out}}{R_F} \quad \dots (1)$$

$$(0 - V_X) A_o = V_{out}$$


$$\therefore \frac{V_1}{R_1} + \frac{V_2}{R_2} + \left(\frac{R_1 + R_2}{R_1 R_2} \right) \cdot \frac{1}{A_o} \cdot V_{out} = -\frac{V_{out}}{R_F} - \frac{1}{R_F A_o} V_{out}$$

$$\therefore V_{out} = - \left[R_F \left(\frac{R_1 + R_2}{R_1 R_2} \right) \frac{1}{A_o} + \frac{1}{A_o} + 1 \right]^{-1} \left(\frac{R_F}{R_1} V_1 + \frac{R_F}{R_2} V_2 \right)$$

→ According to my design:

$$V_{out} = -(18 + 0.001 + 1)^{-1} \times (6V_1 + 12V_2) *$$

2. Integrator:

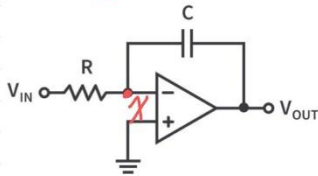

$$\frac{V_{in} - V_X}{R} = \frac{V_X - V_{out}}{1/sC} \quad \therefore \frac{V_{out}}{V_{in}} = \frac{-1}{A_o + (1 + \frac{1}{A_o})RC}$$

According to my design:

$$V_{out} = \frac{-1}{0.001 + 1.001 \times 0.13} V_{in}$$

∴ Over all gain of my design:

$$\frac{V_y(s)}{V_x(s)} = \frac{-\frac{R_F}{R_2}}{\left[\frac{1}{A_o} + \left(1 + \frac{1}{A_o}\right) sRC \right]^2 + \frac{R_F}{R_1}} = \frac{-12}{(10^{-3} + 0.1001s)^2 + 6}$$

By Laplace transform ($V_X(s) = \frac{1}{s}$)

$$V_y(t) = -600000 \left\{ \frac{1}{1200000} - e^{-t/1001 \times RC} \left[\sin\left(\frac{2000\sqrt{3}t}{1001RC}\right) + 200\sqrt{3} \cos\left(\frac{200\sqrt{3}t}{1001RC}\right) \right] \right\}$$

→ we can see there is $e^{-t/1001RC}$ which cause damping,
and also the period is different when we consider finite gain.

Calculation when we consider finite gain